

Seat No: _____

[29]
E/K



Sardar Patel University

No. of Printed Pages: 04

B.Sc Semester-I Examination (On Demand) NC

Subject: Physics Paper Code: US01CPHY02

Title: Network Analysis, Optics and Laser

Date: 16/06/2022 (Thursday)

Time: 09:00 am To 11:00 am

Total Marks: 70

Q.1 Choose correct answer from given options.

(10)

- 1) How many number of independent node equations are required to analyse a network having three junction point and five branches?
(a) 2 (b) 6 (c) 5 (d) 3
- 2) Mesh method of network analysis makes use of the following to analyse a network.
(a) Kirchoff's Voltage Law (b) Kirchoff's Current Law
(c) Faraday's Law (d) Lenz's Law
- 3) In an ac bridge the null detector is usually _____.
(a) a galvanometer (b) an ammeter (c) a head phone (d) a voltmeter
- 4) The capacitive reactance of a capacitor is _____.
(a) $X_C = 1/fC$ (b) $X_C = 1/2\pi fC$ (c) $X_C = 2\pi/fC$ (d) $X_C = 2\pi f/C$
- 5) Wien bridge is used to measure the unknown _____.
(a) resistance (b) reactance (c) frequency (d) capacitance
- 6) The equation for the resolving power of prism is _____.
(a) $t \cdot d\mu / d\lambda$ (b) nN (c) $1.22 \lambda / 2 \sin\alpha$ (d) $a / 1.22 \lambda$
- 7) In Michelson interferometer, circular fringe are obtained if the position of M_1 and M_2' is _____.
(a) perpendicular (b) crossed (c) parallel (d) overlapping
- 8) Einstein's coefficient for stimulated absorption is _____.
(a) A_{12} (b) B_{12} (c) A_{21} (d) B_{21}
- 9) In the CO₂ gas laser which gas used as a coolant.
(a) CO₂ (b) N₂ (c) H₂ (d) He
- 10) A laser system needs _____ mW for writing.
(a) 5 (b) 10 (c) 15 (d) 25

Q.2 Fill in the blanks and True/False

(08)

- 1) _____ current is always flows in clockwise direction. (Mesh, Loop)
- 2) Hay bridge is suitable for the coils having Quality factor _____. ($Q > 10$, $Q < 10$)
- 3) _____ measure the resolving power of grating. ($\lambda / d\lambda$, $n\lambda$)
- 4) _____ light source emits light in all direction. (Ordinary, Laser)
- 5) Superposition theorem is useful in analysing a network containing more than one Voltage sources. (True / False)
- 6) A capacitor offers a high resistance to the high frequency current flowing through it. (True / False)
- 7) The working principle of Jamin's interferometer is based on division of amplitude. (True / False)
- 8) Light Amplification by Stimulated Emission of Radiation is acronym for Laser. (True / False)

①

C.P.T.O

Q.3 Answer the following questions in Short. (Attempt any Ten)

(20)

- 1) State and explain voltage divider theorem.
- 2) State Thevenin theorem.
- 3) Define the term i) Loop ii) Node
- 4) Write the balance conditions for an ac bridge.
- 5) Enlist the possible sources of errors in the Wheatstone bridge measurement.
- 6) Give the names of AC bridges.
- 7) Explain in short resolution and resolving power.
- 8) State the factors on which the R.P of grating depends.
- 9) State Rayleigh criteria for resolving power.
- 10) Define spontaneous emission.
- 11) What are the properties of Lasers?
- 12) Name the different methods of Pumping in laser?

Q.4 Answer the following Long questions. (Attempt any Four)

(32)

- 1) Using Suitable example explain mesh current analysis of three mesh network with circuit diagram.
- 2) Explain Norton theorem in detail.
- 3) Discuss the basic operation of a Wheatstone bridge and derive its balance condition.
- 4) Explain construction and working of Maxwell bridge and derive the equation for unknown inductance.
- 5) State principle of Jamin's interferometer with necessary diagram, explain its application to determine Refractive index of Gas.
- 6) State principle and explain construction and working of Michelson's interferometer.
- 7) Derive relationship between Einstein's coefficient A and B.
- 8) Explain the construction and working of CO₂ Laser

[29]
E+G

સરદાર પટેલ યુનિવર્સિટી
એફ. વાય. બી. એસ્.સી. . સેમેસ્ટર - ૧ ભૌતિકજ્ઞાન (On Demand) NC
વિષય: નેટવર્ક એનાલિસિસ, ઓપ્ટિક્સ અને લેસર

Code: US01CPHY02

કલ ગુણ - ૭૦

તારીખ: ૧૬ - ૦૫ - ૨૦૨૨ , ગુરુવાર

समय : ०८-०० थी ११-००

પ્રક્ષા - ૧ નીચેના પ્રશ્નોમાંથી યોગ્ય વિકલ્પ પસંદ કરો

(90)

પ્રક્ષ- ૨ નીચેની ખાલીજગ્યાપૂરો તથા વિધાનો સાચા છે કે ખોટા તે જણાવો

(06)

- _____ પ્રવાહ હુમેશા સમઘડી દિશામાં વહે છે. (મેશ, લૂપ)
 - ગુંચળાના _____ અવધિના ગુણવત્તા એંક (Q) માટે હે બ્રિજ નો ઉપયોગ થાય છે. ($Q > 10$, $Q < 10$)
 - _____ વડે ગ્રેટિંગની (Grating) વિભેદન શક્તિ માપી શકાય. (λ / $d\lambda$, $n\lambda$)
 - પ્રકાશનો સ્કોર્ટ (Light Source) બધી દિશાઓમાં પ્રકાશને ઉત્સર્જિત કરે છે. (સામાન્ય, લેસર)

૫. અધ્યારોપણનું પ્રમેય એક થી વધુ વોલ્ટેજ ઉદગમ પ્રકારના જાળતંત્ર માટે ઉપયોગી છે. (સાચું, ખોટું)
૬. કેપેસિટર તેમાંથી પસાર થતા ઉંચી આવૃત્તિના વિદ્યુતપ્રવાહ માટે વધુ મૂલ્યનો અવરોધ પૂરો પડે છે.(સાચું, ખોટું)
૭. જેમીન ઇન્ટરફેરોમીટર કંપિસ્ટારના વિભાજનના સિદ્ધાંત પાર કાર્ય કરે છે.(સાચું, ખોટું)
૮. લેસરનું પુરુણામ Light Amplification by Stimulated emission of Radiation છે.(સાચું, ખોટું)

પ્રશ્ન- ૩ કોઈપણ દસ (૧૦) પ્રશ્નોના જવાબ સંક્ષિપ્તમાં લખો

(૨૦)

૧. આકૃતિ સાથે વોલ્ટેજ ભાજક પ્રમેય લખો.
૨. થેવેનિન પ્રમેયનું કથન લખો.
૩. વ્યાખ્યા આપો i) બંધ ગાળો (Loop) ii) મધ્યવર્તી (Node)
૪. A.C. બ્રિજના સંતુલનની શરત લખો.
૫. વહિસ્ટનબ્રિજથી થતા માપનમાં ઉદ્ભવતી ત્રુટિઓની યાદી ટ્રૂકમાં જણાવો.
૬. A.C. બ્રિજના નામ જણાવો.
૭. વિભેદન અને વિભેદન શક્તિ ટ્રૂકમાં સમજાવો.
૮. ગ્રેટિંગની વિભેદન શક્તિ કઈ કઈ બાબતો પર આધાર રાખે છે.
૯. વિભેદન શક્તિમાટે રેલેનું પ્રમાણ સમજાવો.
૧૦. તત્ક્ષણ ઉત્સર્જનની (Spontaneous Emission) વ્યાખ્યા આપો.
૧૧. લેસરના ગુણધર્મો જણાવો.
૧૨. લેસર માટે પમ્પિંગની અતિગ રીતોના નામ લખો.

પ્રશ્ન-૪ કોઈપણ ચાર (૪) પ્રશ્નોના જવાબ વિસ્તૃતમાં લખો.

(૩૨)

૧. ત્રણ જાળીવાળા જાળતંત્રનું જાળીપ્રવાહની રીતનું કૃતિ દ્વારા વિશ્લેષણ સમજાવો.
૨. નોર્ટનનું પ્રમેય જરૂરી આકૃતિ દોરીને સમજાવો.
૩. વહિસ્ટનબ્રિજ પરિપથનું મૂળભૂત કાર્ય જરૂરી વિદ્યુત પરિપથ દોરીને સમજાવો અને બ્રિજ સંતુલનની જરૂરી શરત માટેનું સમીકરણ તારવો.
૪. મેક્સવેલબ્રીજ પરિપથની રચના અને કાર્ય સમજાવી તેના વડે ગુંચળાનું અજ્ઞાત ઈંડકટન્સ શોધવાની રીત સમજાવો.
૫. જેમીન ઇન્ટરફેરોમીટરનો સિદ્ધાંત, રચના અને કાર્ય પદ્ધતિ આકૃતિ દોરી સમજાવો અને વાયુ નો વકીભવનાંક શોધવા માટે જેમીન ઇન્ટરફેરોમીટરનો ઉપયોગ ચર્ચો.
૬. માઇકલસન ઇન્ટરફેરોમીટરનો સિદ્ધાંત, રચના અને કાર્ય પદ્ધતિ સમજાવો.
૭. આઈન્સ્ટાઈનના સહગુણકો A અને B વચ્ચેનું સબંધ દર્શાવતું સમીકરણ મેળવો.
૮. જરૂરી આકૃતિ દોરી CO_2 લેસરની રચના અને કાર્યપદ્ધતિ સમજાવો.