



SEAT No. _____

No. of Printed Pages: 2

[57]

SARDAR PATEL UNIVERSITY

S. Y. B.Sc. Examination, Semester III

Date & time: ૩૫૧૦, 16th 2022 (Thursday), 12:00 p.m. to 02:00 p.m.

Applied Physics, Course Code- US03CAPH22

Course title- Digital electronics and optoelectronic devices

Maximum Marks: 70

Q-1 Write answers to the following multiple-choice questions in your answer book by selecting the proper option. [10]

- (1) The Exclusive-OR gate law states that-

(A) $\bar{A}B + A\bar{B}$	(C) $AB + \bar{A}\bar{B}$
(B) $\bar{A}B + \bar{A}\bar{B}$	(D) $AB + \bar{A}B$
- (2) The 2's complement of the binary number 10101011 is-

(A) 01010101	(C) 10101000
(B) 01010100	(D) 11110000
- (3) In the binary numbers the position of signed number is fixed at the

(A) Most significant bit	(C) Least significant bit
(B) both a and b	(D) Not fixed
- (4) The logic expression $(A + B)(\bar{A} + \bar{B})$ can be implemented by giving the inputs A and B to a two-input

(A) NOR gate	(C) X-NOR gate
(B) NAND gate	(D) X-OR gate
- (5) The number of cells in a 5 variable K-map is -

(A) 6	(C) 36
(B) 12	(D) 32
- (6) Both the J-K and T flip flop are derived from:

(A) The basic SR latch	(C) both a and b
(B) The basic D latch	(D) None of these
- (7) Which of the following logic circuits accepts two binary digits on inputs, and produces two binary digits, a sum bit and a carry bit on its outputs?

(A) Full-adder	(C) Serial adder
(B) half-adder	(D) parallel adder
- (8) A binary to octal decoder is

(A) 3 line to 8 line decoder	(C) 4 line to 8 line decoder
(B) 1 line to 8 line decoder	(D) Any line to 8 line decoder
- (9) A photo-diode is normally:

(A) Forward biased	(C) Reverse biased
(B) Neither forward nor biased	(D) Emitting light
- (10) The power consumption of an LCD as compared to an LED is:

(A) Same	(C) Less
(B) More	(D) Can't be defined

Q-2 Fill in the blanks/ True- False (All questions are compulsory)

[08]

- (1) In an LED emission of light is due to emission of electrons. [True/ False]
- (2) In a phototransistor, the base current is inversely proportional to the light. [True/ False]
- (3) A byte is a group of 8 bit. [True/ False]
- (4) The octal code is used for the labelling of K-map. [True/ False]
- (5) In X-NOR gate, both the inputs are high then the output is
- (6) An n variable K- map have ... cells.
- (7) gate is used in parity bit checker.
- (8) For a Light Emitting Diode, Semiconductor material is used.

P.T.O.

Q-3 Short questions (Attempt any ten out of twelve)

[20]

- (1) State the De Morgan's theorem.
- (2) What is the difference in between Flip Flop and latch?
- (3) Convert the $(1101.00010101)_2$ to decimal.
- (4) Brief note on laws of Boolean Algebra.
- (5) Find the binary equivalent of $(368)_{10}$.
- (6) Find the $(734)_8 = (?)_{16}$.
- (7) Sketch the half adder diagram.
- (8) Sketch the even parity bit checker diagram.
- (9) Why we need the semiconductor material for a specific band gap in case of LED?
- (10) What is the function of multiplexer?
- (11) Brief the optocoupler.
- (12) What are optoelectronic devices?

Q-4 Long Questions (Attempt any four out of eight, each question has equal marks.)

[32]

- (1) Prove the Boolean expression of Exclusive OR and Exclusive NOR gate using truth table technique.
- (2) Solve the following numbers.
(i) $(111011)_2 - (101101)_2$ (ii) $(ABCD)_{16} = (?)_8$ (iii) $(5867)_8 = (?)_2$ (iv) $(1357)_{10} = (?)_2$
- (3) Prove that
(i) $\overline{ACB} + (A + B + C) = \overline{A}\overline{B}\overline{C}$ (ii) $\overline{\overline{ABC} + \overline{AB} + BC} = \overline{A}\overline{B}$
- (4) What is Flip Flop? Explain the J-K flip flop in detail with appropriate figure.
- (5) What is a parity bit checker? Explain the even and odd parity checker in detail with necessary figure.
- (6) Explain the Decoder in detail with an example.
- (7) What is a Photocell? Explain the Solar cell in detail.
- (8) Write a detail note on Light Emitting Diode's operation and construction and its application.
