

SEAT No. _____

[15]
ECE



No. of Printed Pages: 4

SARDAR PATEL UNIVERSITY

B.Sc. Sixth Semester Examination

PHYSICS [US06CPHY05]

Digital Electronics, Electronics Communication and VLSI Technology

Tuesday, 04/10/2022

Time: - 3:30 PM To 5:30 PM

Total Marks: - 70

- N.B (i) All the symbols have their usual meanings.
(ii) Figures at the right side indicate full marks.

Q1 Choose the correct Option. (Attempt all)

[10]

1. What is the Binary equivalent of 22D?
(a) 0001 0110B (b) 0001 0111B (c) 0001 1000B (d) 0010 0010B
2. The group of four binary bits is called _____
(a) Word. (b) Byte. (c) Nibble. (d) Bit.
3. Which of the following is equivalent to the AND gate with inverters at both the inputs?
(a) NOR Gate. (b) NAND Gate. (c) XOR Gate. (d) OR Gate.
4. Which of the following flip flop have problem of racing?
(a) RS (b) D (c) JK (d) Master Slave JK
5. What is the natural count of a ripple counter constructed with five JK flip flops?
(a) 32 (b) 31 (c) 30 (d) 16
6. Which multi vibrator can be used as flip flop?
(a) Astable (b) Multistable (c) Monostable (d) Bi stable
7. The process of converting low frequencies signals to high frequencies is known as _____
(a) Amplification. (b) Attenuation. (c) Modulation. (d) Demodulation.
8. The size of antenna can be reduced by keeping carrier frequency _____
(a) Same as audio signal. (b) Very High. (c) Very Low (d) Medium.
9. How many logic gates are integrated on a LSI integrated circuit?
(a) 12 to 100 (b) 101 to 1000 (c) less than 12 (d) more than 1000
10. Which logic family offers low power consumption?
(a) TTL (b) CMOS (c) PMOS (d) NMOS

Q2 Do as Directed. (Attempt all)

[08]

(A) Fill in the blanks with correct answer.

1. _____ and _____ gates are known as universal logic gates.
2. There are _____ bits in an ASCII code.
3. In most of the applications the frequency of carrier is kept _____ than modulating signal
4. The circuit made on single silicon chip is known as _____

- (B) Mention whether the following statements are True or False.**
5. XNOR gate is Universal logic gate.
 6. Synchronous counters are faster than Ripple counters.
 7. AM transmission requires more bandwidth than FM transmission.
 8. The mobility of electrons is higher than holes in silicon semiconductor.

Q3 Answer the following questions in short. (Attempt any ten)

[20]

1. State De Morgan's theorems.
2. Draw the logic symbols of universal gates with their truth tables.
3. Convert Decimal 127 in Binary and Hexadecimal numbers.
4. What is truth table? Write it for JK and JK Master slave flip flops.
5. What is the racing in the function of a flip flop?
6. Briefly explain function of D flip flop with truth table and timing diagrams.
7. Define Modulation processes and give classification of various modulation process.
8. Explain advantages of frequency modulation process in communication system.
9. Briefly explain Simplex and Duplex communication.
10. Give general classification of Integrated circuit.
11. Give the cross sectional view of the PMOS structure fabricated on IC.
12. What do you mean by CMOS? Draw the basic CMOS inverter circuit and explain it.

Q4 Answer the following questions in details. (Attempt any four)

[32]

1. Draw the logic symbol and circuit of XOR and XNOR gates and explain them.
2. Draw the symbol and truth table of NAND gate and write a note on TTL NAND gate.
3. Draw the circuit for four bit Shift right register and explain its working with necessary wave forms and truth table.
4. Draw the circuit of 4 bit ripple counter and explain its working with wave diagrams and truth table.
5. Draw the block diagram of modern electronic communication system and explain function of each block. Also discuss the advantages of modulation process.
6. Define amplitude modulation process, Derive the expression of AM voltage and draw necessary waveforms.
7. Explain basic configurations of transistors used for diode operation in monolithic IC and draw the cross sectional view of various connections.
8. With necessary diagram explain fabrication processes for monolithic planner diode, avalanche diode and schottky diode.

SEAT No. _____

SARDAR PATEL UNIVERSITY
B.Sc. Sixth Semester Examination
PHYSICS [US06CPHY05]



Digital Electronics, Electronics Communication and VLSI Technology
Tuesday, 04/10/2022

Time: - 3:30 PM To 5:30 PM

Total Marks: - 70

- નોંધ: - (1) બધા પ્રતીકોના તેમના સામાન્ય અર્થો છે.
(2) જમણી બાજુના આંકડા કુલ ગુણ દર્શાવે છે.

P.1 સાચો વિકલ્પ પસંદ કરો. (બધાજ જવાબ આપો) [10]

1. દશાંશ ર૨ ની બાઈનરી સમકક્ષ શું છે?
(a) 0001 0110B (b) 0001 0111B (c) 0001 1000B (d) 0010 0010B
2. ચાર ડિસંગી બિટ્સના જીથને _____ કહેવામાં આવે છે.
(a) વર્ડ (b) બાઈટ. (c) નીબલ. (d) બીટ.
3. નીચેનામાંથી કયું બંને ઇનપુટ પર ઇન્વાર્ટર સાથેના એન્ડ ગેટની સમકક્ષ છે?
(a) નોર ગેટ. (b) નેન્ડ ગેટ. (c) એક્સઓર ગેટ. (d) ઓર ગેટ.
4. નીચેનામાંથી કયો ફિલિપ ફલોપ માં રેસિંગની સમસ્યા છે?
(a) આર એસ. (b) ડી (c) જે કે. (d) માસ્ટર સ્લેવ જે કે.
5. પાંચ JK ફિલિપ ફલોપ સાથે બનાવવામાં આવેલા રિપલ કાઉન્ટરની કુદરતી ગણતરી કેટલી છે?
(a) ૩૨ (b) ૩૧ (c) ૩૦ (d) ૧૯
6. ફિલિપ ફલોપ તરીકે કયા મલ્ટી વાઇબ્રેટરનો ઉપયોગ કરી શકાય છે?
(a) એસ્ટેબલ (b) મલ્ટિસ્ટેબલ (c) મોનોસ્ટેબલ (d) ડ્રિ સ્ટેબલ
7. ઓછી ફીકવન્સીના સિઝલોને ઉચ્ચ ફીકવન્સીઝમાં રૂપાંતરિત કરવાની પ્રક્રિયા _____ તરીકે ઓળખાય છે.
(a) એમ્પલીફિકેશન. (b) એટેન્યુએશન. (c) મોડ્યુલેશન. (d) ડિમોડ્યુલેશન.
8. એન્ટેનાનું કે કેરીયરની આવર્તન સંખ્યા _____ રાખીને ઘટાડી શકાય છે.
(a) ઓડિયો સિઝલ જેટલી જ. (b) ખુબ વધારે. (c) ખુબ ઓછી. (d) મધ્યમ.
9. LSI ઇન્જિન્યોરેડ સર્કિટ પર કેટલા લોજિક ગેટ એક્સિટ કરેલા હોય છે?
(a) ૧૨ થી ૧૦૦ (b) ૧૦૧ થી ૧૦૦૦ (c) ૧૨ કરતા ઓછા (d) ૧૦૦૦ થી વધારે
10. કયો લોજિક પરિવાર ઓછો વીજ વપરાશ કરે છે?
(a) TTL (b) CMOS (c) PMOS (d) NMOS

P.2 નિર્દેશ મુજબ કરો. (બધાજ જવાબ આપો) [06]

(A) સાચા જવાબ સાથે ખાલી જગ્યાઓ ભરો.

1. _____ અને _____ ગેટ્સ યુનિવર્સલ લોજિક ગેટ તરીકે ઓળખાય છે.
2. ASCII કોડમાં કુલ _____ બિટ્સ હોય છે.
3. મોટાભાગની એપ્લિકેશનોમાં મોડ્યુલેટીંગ સિઝલ કરતાં વાહક સિઝલ ની આવર્તન સંખ્યા _____ રાખવામાં આવે છે
4. સિંગલ સિલિકોન ચિપ પર બનેલ સર્કિટ _____ તરીકે ઓળખાય છે.

- (B) નીચેના વિધાન સાચા છે કે ખોટા છે તેનો ઉત્ત્વેભ કરો.
- પ. એક્ઝનોર લોજિક ગેટ યુનિવર્સલ ગેટ તરીકે ઓળખાય છે.
 - ગ. સિંકોનસ કાઉન્ટર્સ રિપલ કાઉન્ટર્સ કરતાં વધુ અડપી છે.
 - હ. એએમ ટ્રાન્સમિશનને એફ્મ ટ્રાન્સમિશન કરતાં વધુ બેનવિદ્યથની જરૂર પડે છે.
 - ચ. ઇલેક્ટ્રોનની ગતિશીલતા સિલિકેન સેમિકન્કટરમાં હોલ્સ કરતાં વધુ છે.
- પ.૩ નીચેના પ્રશ્નોના દ્રુકમાં જવાબ આપો. (કોઈપણ દસના જવાબ આપો)
૧. ડી મોર્ગનના પ્રમેય લખો.
 ૨. યુનિવર્સલ લોજિક ગેટ તેમના પ્રતીકો અને સત્ય કોષ્ટકો (દુથ ટેબલ) સાથે દોરો.
 ૩. દશાંશ ૧૨૭ ને બાઈનરી અને હેક્સાડેસિમલ સંપ્રામાં કન્વર્ટ કરો.
 ૪. સત્ય કોષ્ટકો (દુથ ટેબલ) શું છે? તેને JK અને JK માસ્ટર સ્લેવ ફિલિપ ફ્લોપ્સ માટે લખો.
 ૫. ફિલિપ ફ્લોપના કાર્યમાં રેસિંગ એટલે શું છે?
 ૬. સત્ય કોષ્ટક (દુથ ટેબલ) અને સમય આફ્ટિઓ સાથે D ફિલિપ ફ્લોપનું કાર્ય સંક્ષિપ્તમાં સમજાવો.
 ૭. મોડયુલેશન પ્રક્રિયાઓને વ્યાખ્યાયિત કરો અને વિવિધ મોડયુલેશન પ્રક્રિયાનું વર્ગીકરણ આપો.
 ૮. કોમ્યુનિકેશન સિસ્ટમાં ફીડવન્સી મોડયુલેશન પ્રક્રિયાના ફાયદા સમજાવો.
 ૯. સિમ્પલેક્સ અને ડુપ્લેક્સ કોમ્યુનિકેશનનાં સંક્ષિપ્તમાં સમજાવો.
 ૧૦. ઇન્ટિગ્રેટડ સકિટનું સામાન્ય વર્ગીકરણ આપો.
 ૧૧. ઇન્ટિગ્રેટડ સરકીટ પર બનાવાયેલ PMOS સ્ટ્રક્ચરનો કોસ સેક્શનલ વ્યુ આપો.
 ૧૨. CMOS માટે તમારો અર્થ શું છે? મૂળભૂત CMOS ઇન્વાર સકિટ દોરો અને તેને સમજાવો.
- પ.૪ નીચેના પ્રશ્નોના વિગતવાર જવાબ આપો. (કોઈપણ ચાર ના જવાબ આપો) [૩૨]
૧. એક્ષ ઓર અને એક્ષ નોર ગેટસના લોજિક સિમ્બોલ અને સકિટ દોરો અને તેમને સમજાવો.
 ૨. NAND gate. NAND ગેટનું પ્રતીક અને સત્ય કોષ્ટક (દુથ ટેબલ) દોરો અને TTL NAND પર નોંધ લખો.
 ૩. ચાર બીટ જમણા શિફ્ટ રજીસ્ટર માટે સકિટ દોરો અને જરૂરી વેવ સ્વરૂપો અને સત્ય કોષ્ટક (દુથ ટેબલ) સાથે તેનું કાર્ય સમજાવો.
 ૪. ૪ બીટ રિપલ કાઉન્ટરનું સકિટ દોરો અને તરંગ આફ્ટિઓ અને સત્ય કોષ્ટક સાથે તેનું કાર્ય સમજાવો.
 ૫. આધુનિક ઇલેક્ટ્રોનિક કોમ્યુનિકેશન સિસ્ટમનો બ્લોક ડાયાગ્રામ દોરો અને દરેક બ્લોકની કામગીરી સમજાવો. મોડયુલેશન પ્રક્રિયાના ફાયદાઓની પણ ચર્ચા કરો.
 ૬. એમ્પલીન્યુંડ મોડયુલેશન પ્રક્રિયાને વ્યાખ્યાયિત કરો, એમ વોલ્ટેજની અભિવ્યક્તિ (સમીક્રરણ) મેળવો અને જરૂરી વેવફોર્મ્સ દોરો.
 ૭. મોનોલિથિક IC માં ડાયોડ માટે ઉપયોગમાં લેવાતા ટ્રાન્ઝિસ્ટરના મૂળભૂત ઉપરખાંકનો સમજાવો અને વિવિધ જોડાણોના કોસ સેક્શનલ વ્યુ દોરો.
 ૮. જરૂરી આફ્ટિ સાથે મોનોલિથિક પ્લાનર ડાયોડ, એવેલેચ ડાયોડ અને સ્કોર્ટકી ડાયોડ માટે ફિલ્ટરેક્શન પ્રક્રિયાઓ સમજાવો.