

[42]

Roll No. _____

No. of Printed Pages: 02



SARDAR PATEL UNIVERSITY

BCA Semester-3 Examination, 202

US03SBCA21 || DIGITAL COMPUTER ELECTRONICS

17th June, 2022

Friday

Time : 12.00 p.m. – 03.00 p.m.

Marks: 35

Q-1 **Select the appropriate option for the following questions:** **05**

- 1) The OR gate has two or more input signals. If any input is _____, the output is high.

A. High	C. Both A and B
B. Low	D. None
- 2) In k-map, pair eliminates _____ variable.

A. One	C. Two
B. Three	D. Four
- 3) A combinational circuit that performs the arithmetic addition of two bits is called _____.

A. full adder	C. binary adder
B. half adder	D. decoder
- 4) A _____ register is the simplest kind of register; all it does store a digital word.

A. shift left	C. buffer
B. shift right	D. counter
- 5) The _____ gate has two or more input signals. All inputs must be high to get a high output.

A. NAND	C. AND
B. OR	D. NOR

Q-2 **Tick (TRUE or FALSE) and Fill in the blanks.** **04**

- 1) De Morgan's second theorem says that a NAND gate is equivalent to a bubbled NAND. [TRUE/FALSE]
- 2) A Decoder is a combinational circuit that converts binary information from the n coded inputs to a maximum of 2ⁿ unique outputs. [TRUE/FALSE]
- 3) A _____ is logic circuit that can add two binary numbers.
- 4) A register is a group of _____ that work together as a unit.

Q-3 **Give short answers of the following questions: (ANY FIVE)** **10**

- 1) Explain Associative law.
- 2) Describe the AND, NOR gate.
- 3) Draw the circuit diagram of comparator.
- 4) Define the function of Encoder and Decoder.
- 5) What is Multiplexer?
- 6) Differentiate between Half adder and Full adder.
- 7) What is register? Draw circuit diagram of shift right register.
- 8) Define Flip flop. What is Race condition?

①

(P.T.O)

Q-4

Give Long answers of the following questions: (ANY FOUR)

16

- 1) Explain De Morgan's first theorem.
- 2) Explain truth table with appropriate example.
- 3) Explain 8x3 line encoder in detail.
- 4) What is k-map? Explain pair and quad with example.
- 5) Explain full adder in detail.
- 6) Explain 4x1 multiplexer in detail.
- 7) Explain shift left register.
- 8) Explain 4-bit binary Adder / Subtractor.

