

(146A-12) Seat No. _____

No. of printed pages : 2

SARDAR PATEL UNIVERSITY
B.C.A. (1st Semester) (CBCS) Examination 2016
Wednesday, 16th November
10:00 am to 12:00 Noon
US01EBCA01 || Digital Computer Electronics

Total Marks: 70

Q:1 Select an appropriate answer for the following. **[10]**

1. The OR gate has two or more input signals. If any input is _____, the output is high.
a). High b). Low c). Both A and B d). None
2. An invert gate is also called a _____ gate.
a) NOR b) NOT c) XNOR d) NAND
3. The _____ gate has two or more input signals. All inputs must be same to get a high output.
a). EX-OR b). NAND c). EX-NOR d). NOR
4. In Comparator, _____ gate is use for comparing bits in word.
a) XOR b) AND c) NOR d) XNOR
5. In k-map, octets eliminates _____ variable.
a)One b) Two c) Three d) Four
6. Half adder is logic CKT that adds _____ digit at a time.
a) 1 b) 2 c) 3 d) 4
7. A combinational circuit that performs the arithmetic addition of two bits is called _____
a) Half Adder b) Full Adder c) Binary Adder d) Decoder
8. In half adder XOR gate's output _____
a)Carry b)Sum c) Reminder d) None
9. A _____ register is the simplest kind of register; all it does store a digital word.
a) shift left b) shift right c) buffer d) simple
10. In D flip-flop, when CLK is high then input is _____.
a) high b) low c) invert of input d) same as input

①

[P.T.O]

Q:2 Answer the following questions. (Attempt any ten) [20]

1. Explain OR gate in detail .
2. Explain Commutative Law.
3. Write truth table for : $A'B+B'C$
4. Explain De-Morgan's first theorem.
5. Simplify using K-Map: $F(A,B,C)=\sum(1,2,5)$
6. Draw the circuit diagram for 4 * 1 multiplexer.
7. Describe Quad in K-Map.
8. Explain D Flip-Flop.
9. Define Comparator in short.
10. What is shift register? Give its type.
11. Explain logical addition in Boolean algebra.
12. Explain Binary adder in short.

Q:3 What is Truth Table? Explain Associative, Commutative and Distributive laws with example. [10]

OR

Q:3 What is Gate? Explain NAND, NOR, AND, EX-OR with diagram and truth table. [10]

Q:4 A. What is Karnaugh – Map ? [05]

Simplify using k- map: $F(A,B,C,D)=\sum(1,3,5,6,8,11,13)$

B. Explain 8*3 line encoder in detail. [05]

OR

Q:4 A. Explain two variables and three variables k-maps with example. [05]

B. Explain Comparator with circuit and example. [05]

Q:5 A. Explain Binary Adder with circuit diagram and example. [05]

B. What is Multiplexer? Explain 8 * 1 with logic circuit and truth table [05]

OR

Q:5 A. Explain binary adder-subtractor in detail. [05]

B. Explain Binary Adder with circuit diagram and example. [05]

Q:6 A. Explain D Flip-Flop with proper circuit diagram. [05]

B. Explain Shift Left register with example. [05]

OR

Q:6 A. Explain Controlled Buffer register with example. [05]

B. Explain Ring counter with appropriate example [05]

~~~~~ Best Of Luck ~~~~~

— X —  
②