

[14/A4]

SEAT No. _____

No. of Printed Pages : 2

SARDAR PATEL UNIVERSITY
External Examination
F.Y.BCA (Sem-1) NC [old Course]
US01EBCA01: Digital Computer Electronics
Time: 10.00 am – 12.00 noon

Date: 23/10/2018, Tuesday

Marks: 70

Q-1 Select the correct option from the following questions.

10

- 1 The _____ gate has two or more input signals. All inputs must be high to get a high output.
A. AND B. NOT C. NOR D. NAND
- 2 De Morgan's first theorem says that a NOR gate is equivalent to a _____.
A. bubbled OR B. bubbled NOR C. bubbled AND D. AND bubbled
- 3 In Comparator, _____ gate is use for comparing bits in word.
A XOR B AND C NOR D XNOR
- 4 2. In k-map, quad eliminates _____ variable.
A. one B. two C. three D Four
- 5 A combinational circuit that performs the arithmetic addition of three bits is called _____.
A Full Half adder B Half adder C Binary adder D Decoder
- 6 In half adder XOR gate's output is _____.
A. carry B. sum C. reminder D. none
- 7 In shift right register, the arrival of the first rising clock edge sets the _____ flip-flop.
A. left B. right C. up D. down
- 8 Ring counter producing words with 1 high bit, which shifts _____ position per clock pulse
A. one B. two C. three D. none
- 9 A _____ is a memory element that stores a binary digit.
A. Binary adder B. Decoder C. Multiplexer D. Flip flop
- 10 A gate is a logic circuit with one or more input signals but only _____ output signal.
A. two B. one C. three D. four

Q-2 Answer the following questions. (ATTEMPT ANY TEN)

20

- 1 Describe the AND, NOR gate.
- 2 Explain Associative law.
- 3 Write truth table for : $ABC + A'B'C'$

(1)

(P.T.O.)

- 4 Explain product of sum.
- 5 Describe pair in k-map
- 6 Define comparator in short.
- 7 Draw the circuit diagram of Half Adder.
- 8 Describe binary subtractor in short.
- 9 Define Multiplexer. What is the use it?
- 10 Define : register and shift register. What are the types of shift register?
- 11 Explain D flip-flop.
- 12 Draw the circuit diagram of Controlled Buffer Register.

- Q-3** **A** Write note on: De'Morgan's first theorem. **5**
 B Explain AND, NOT gates. **5**

OR

- Q-3** **A** Write note on: De'Morgan's second theorem. **5**
 B Explain Associative law. **5**

- Q-4** **A** Explain 8x3 line Encoder in detail. **5**
 B What is k-map? Explain pair with example. **5**

OR

- Q-4** **A** Explain 3x8 line Decoder in detail. **5**
 B Explain comparator. **5**

- Q-5** **A** Explain Half adder in detail. **4**
 B Explain 4x1 Multiplexer. **6**

OR

- Q-5** **A** Explain Full adder in detail. **4**
 B Explain 4 bit Binary Subtractor with circuit diagram. **6**

- Q-6** Explain Shift Left and Shift Right Registers in detail. **10**

OR

- Q-6** Explain Ring Counters. **10**

