

SARDAR PATEL UNIVERSITY

B.C.A. (Sem- 3)

US03SBCA21: Digital Computer Electronics

Time: 02.00 pm – 04.00 pm

Marks: 35

Date: 25-11-2019
Monday

Q-1 Select the correct option from the following questions. (05)

- 1) The NAND gate has two or more input signals. If all inputs are _____, the output is low.
A. low B. high C. both A and B D. none
- 2) _____ is a way to simplify the equation.
A. Boolean Algebra B. K-MAP C. Both D. None
- 3) A _____ is a combinational circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.
A. Half Adder B. Decoder C. Encoder D. Comparator
- 4) In D flip-flop, when CLK is high then output is _____.
A. high B. low C. invert of input D. same as input
- 5) A _____ register is the simplest kind of register; all it does is store a digital word.
A. shift left B. shift right C. buffer D. simple

Q-2 Do as directed. (ATTEMPT ANY FIVE) (10)

- 1) Explain De Morgan's first theorem.
- 2) Describe AND and NOR gate.
- 3) What is an octet in k-map?
- 4) Define a Flip-flop. What is a Race Condition?
- 5) Describe in brief about Half Adder.
- 6) Define comparator in short.
- 7) Explain controlled buffer register in short.
- 8) Explain ring counter in short.

Q-3 A Explain associative and commutative law. (05)

B What is k-map? Explain pair and quad with example. (05)

OR

Q-3 A Describe 8*3 line encoder in detail with truth table and diagram. (05)

B Prove that $ABC' + ABC = AB$ using truth table. (05)

- Q-4 A Explain D flip-flop in detail. (05)
B Explain full adder in detail with proper diagram. (05)

OR

- Q-4 A Explain shift left and shift right register. (05)
B Explain 4x1 multiplexer in detail (05)

— X —
②