

SARDAR PATEL UNIVERSITY
TY BSc (V SEM.) (CBCS) EXAMINATION
Monday, 26th November 2012
2.30 pm - 5.30 pm
US05CELC01 : Electro. & Communication
Analog Circuit Design & Its Application

Total Marks: 70

Note: Figures to the right indicate full marks.

- Q.1 Choose correct answer: [10]
- (1) Class AB operation is often used in power amplifier in order to _____.
(a) Overcome Distortion (b) Remove even harmonics
(c) Coet maximum efficiency (d) None
 - (2) In _____ Amplifier the current flows only during positive half cycle.
(a) Class AB (b) Class C
(c) Class B (d) None of these
 - (3) Voltage series feedback results in _____.
(a) Increase both the impedance
(b) Decrease both the impedance
(c) Increase band-width
(d) None of these
 - (4) The efficiency of Class B amplifier is _____ %.
(a) 65 (b) 50
(c) 78.5 (d) None of above
 - (5) _____ is commonly used in a local oscillator in Radio receiver.
(a) Phase shift oscillator (b) Crystal oscillator
(c) Hartly oscillator (d) None of these
 - (6) In a single RC network _____ phase shift obtained.
(a) =90° (b) >80°
(c) >90° (d) <90°
 - (7) WEIN bridge is _____ bridge.
(a) AC (b) DC
(c) AC & DC (d) None of these
 - (8) 555 Timer has high temperature stability that is _____.
(a) -55 to 125 degree (b) -55 to 155 degree
(c) -50 to 125 degree (d) 55 to 125 degree
 - (9) 555 Timer IC's available in
(a) 8 Pin DIP Package (b) 8 Pin Circular Package
(c) 14 Pin DIP Package (d) None of above
 - (10) Astable multivibrator has _____ stable state.
(a) 0 (b) 1
(c) 2 (d) 4

- Q.2 Answer in short. **(Any Ten)** [20]
- (1) Differentiate between Class A and Class AB amplifier.
 - (2) Define cross over distortion.
 - (3) What do you mean by Harmonic distortion ?
 - (4) State advantages of feedback in amplifier.
 - (5) Differentiate between Positive and Negative feedback.
 - (6) Discuss Miller's effect.
 - (7) Define an Oscillator.
 - (8) List out salient features of 555 IC.
 - (9) Define a flip-flop.
 - (10) Differentiate between RC and LC oscillator.
 - (11) Differentiate between Astable and Monostable multivibrator.
 - (12) Draw Pindigram of 555 Timer IC.
- Q.3
- (a) List out different types of amplifiers. [03]
 - (b) Discuss Push-Pull amplifier in detail with necessary diagrams. [07]
- OR**
- Q.3 What do you mean by Power amplifier? Explain working of Class A amplifier with circuit diagrams. [10]
- Q.4 Derive equations for input resistance of Series voltage, Series current and Shunt voltage in feedback amplifier. [10]
- OR**
- Q.4 Discuss concept of output resistance of different types of feed-back network in Amplifier. [10]
- Q.5
- (a) State principle of oscillator and discuss classification of oscillator. [04]
 - (b) Describe in detail construction and working of RC phase shift oscillator. [06]
- OR**
- Q.5
- (a) Discuss construction and working of Colpitt's oscillator. [06]
 - (b) Discuss concept of oscillator stability. [04]
- Q.6 Describe constructional and working mechanism of Astable multivibrator using 555 Timer IC. State its applications. [10]
- OR**
- Q.6 Draw functional block diagram of 555 Timer IC and discuss each section of it. [10]
