

CA

[15]

SARDAR PATEL UNIVERSITY
BSc (V Sem.) Examination
Wednesday, 20 November 2013
10.30 am– 1.30 pm
US05CELE04 – Electronics
Instrumentation I

No. of printed pages: 2

Total Marks: 70

Note: Figures to the right indicate full marks.

- Q.1 Multiple choice questions. [10]
- (1) Maxwell bridge is used to find Inductance of _____
(i) High Q coil (ii) Medium Q coil
(iii) Low Q coil
- (2) The modification applied to Hay bridge to measure high Q coil is _____
(i) connecting a resistor in series to capacitor in arm 1
(ii) connecting a resistor in parallel to capacitor in arm 1
(iii) none of above
- (3) A DC bridge can measure _____
(i) Unknown Capacitance
(ii) Unknown inductance
(iii) Unknown resistance
- (4) A bridge is said to be in balance condition when _____
(i) Minimum current flows through the detector
(ii) Maximum current flows through the detector
(iii) No current flows through the detector
- (5) The power factor of series RC combination is defined as the _____ of the phase angle of the circuit.
(i) cotangent (ii) cosine (iii) none of above
- (6) The _____ is used in audio and HF Oscillators as the frequency determining element.
(i) Schering Bridge (ii) Wein Bridge (iii) Hay Bridge
- (7) Which force summing device is used in capacitive transducer?
(i) Diaphragm (ii) Bourdon Tubes (iii) Mass Cantilever
- (8) The capacitance of the capacitor varies _____
(i) Directly as distance between two conducting plates of capacitor
(ii) Inversely as distance between two conducting plates of capacitor
(iii) None of above
- (9) Which transducer has a very good high frequency response?
(i) Potentiometric (ii) Piezoelectric (iii) Photo electric
- (10) Which resistance wire has an excellent stability and high resistance to fatigue at elevated temperature?
(i) Platinum Tungsten (ii) Constantan (iii) Nichrome

[20]

Q.2 Answer **Any Ten** in brief.

- (1) Draw the circuit of Kelvin bridge and mention balanced condition of the same.
- (2) State two conditions to be satisfied simultaneously to balance an ac bridge.
- (3) Maxwell bridge is suitable for measurement of low Q coil. Explain.
- (4) State applications of Wein bridge.
- (5) State two differences between Hay bridge and Maxwell bridge.
- (6) Draw the circuit diagram of Wein bridge circuit.
- (7) Write three major elements classified by transducer and write the function of it.
- (8) Write the question which can arise for the selection of transducer.
- (9) Write the techniques used to reduce the measurement of error in a transducer.
- (10) Explain the Piezoelectric transducer.
- (11) What is function of each block of instrumentation system?
- (12) Write the relation between stress and strain given by the Hooke's law.

Q.3 Draw the circuit diagram of Maxwell bridge and explain the balance condition for it. [10]

OR

Q.3 Draw the circuit diagram of Kelvin bridge and also explain Kelvin double bridge for finding low value of resistance. [10]

Q.4 Describe in detail Schering bridge and show that the dial of Schering bridge can be calibrated directly in terms of dissipation factor D. [10]

OR

Q.4 Draw the circuit diagram of Hay bridge and explain it. [10]

Q.5 Write a note on classification of transducers. [10]

OR

Q.5 Write a note on LVDT and explain the displacement measurement using two differential transformers. [10]

Q.6 Discuss in detail the thermocouple. [10]

OR

Q.6 Write a note on thermistor and also explain the characteristics of thermistor. [10]

* * *