

SARDAR PATEL UNIVERSITY

B.Sc.(ELECTRONICS) SEM.-5

EXAMINATION -NOV.-2013

INDUSTRIAL ELECTRONICS PAPER-1

SUB CODE: US05CELE05

DATE: 22 NOV. 2013

TIME: 10:30 AM TO 1:30 PM

DAY: FRIDAY

TOTAL MARKS: 70

Q. 1 Choose the correct answer.**[10]**

- (1) Recommended method to TURN-ON SCR is _____.
- (A) Triggering by D.C signal (C) Triggering by A.C signal
(B) Both (A) &(B) (D) None of above
- (2) _____ Connection of SCR used for controlling very high voltage.
- (A) Series (C) Parallel
(B) Bi-directional (D) None of above
- (3) V_{BO} in SCR refer as _____.
- (A) Break down voltage (C) Break over voltage
(B) Over voltage (D) None of above
- (4) UJT mainly used for _____.
- (A) Amplifier (C) Power controlling
(B) Relaxation oscillator (D) None of above
- (5) SCR _____ type of device.
- (A) Uni-directional (C) Multi-directional
(B) Bi-directional (D) None of above
- (6) Thyristor device mainly used for _____.
- (A) Rectification (C) Amplification
(B) Power controlling (D) None of above
- (7) SUS means _____.
- (A) Silicon uniport switch (C) Silicon unmatched switch
(B) Silicon unilateral switch (D) None of above
- (8) TRIAC used for _____.
- (A) Rectification (C) Phase controlling
(B) Generator (D) None of above
- (9) D.C motor consists of _____.
- (A) TRIAC (C) Rotor
(B) Amplifier (D) None of above
- (10) Stepper motor used for _____ speed variation .
- (A) Linear (C) Discrete
(B) Constant (D) None of above

Q.2 Answer the following in short.(any ten)**[20]**

- (1) Define holding current I_h .
- (2) State function of gate in SCR.
- (3) Define reverse recovery current I_{RR} .
- (4) Define string efficiency.
- (5) Differentiate between semiconductor and thyristor device
- (6) State any three important applications of thyristor device.
- (7) Differentiate between DIAC and TRIAC.
- (8) What do you mean by power controlling action?
- (9) State impotence of overvoltage protector circuit.
- (10) Differentiate between D.C motor and Stepper motor.
- (11) State principle of operation of stepper motor.
- (12) Briefly discuss function of shaft in a motor.

ANALYTICAL SKILLS TEST

- Q.3 (A) Discuss the principle of operation and characteristics of SCR. [07]
(B) State important points for designing gate control circuit. [03]
OR
- Q.3 (A) Discuss different methods of turning on a SCR with TURN-ON characteristics. [06]
(B) Discuss TURN-OFF mechanism of SCR. [04]
- Q.4 (A) Explain series operation of SCR with necessary diagram. [07]
(B) Briefly discuss concept of string efficiency. [03]
OR
- Q.4 (A) Discuss the parallel operation of SCR with necessary diagram. [06]
(B) Explain different triggering techniques of parallel connected SCR. [04]
- Q.5 (A) Discuss application of thyristor device as overvoltage protection circuit. [05]
(B) Discuss triggering modes of TRIAC. [05]
OR
- Q.5 (A) Discuss characteristics and operation of UJT with necessary diagram. [05]
(B) Discuss the concept of UJT as relaxation oscillator. [05]
- Q.6 (A) Draw schematic diagram of D.C motor and discuss its working. [06]
(B) Write short note on stepper motor. [04]
OR
- Q.6 (A) Discuss series inverter giving necessary diagram and wave forms. [05]
(B) Define inversion action. Briefly discuss single phase half bridge inverter. [05]