

[22]

No. of Printed Pages: 2

SARDAR PATEL UNIVERSITY
B.Sc. Examination - 2013 [CBCS]
US05CINS04 - Programmable Logic Controller (PLC) – I
20TH November, 2013, 10:30 am - 1:30 pm

Maximum Marks: 70

Que 1 Multiple choice questions.

[10]

- 1 _____: a state in which the machine is performing the task for which it is designed.
 - i. ON
 - ii. RUN
 - iii. JOG
 - iv. None of the above
- 2 _____ switches are not operator accessible.
 - i. Selector
 - ii. Palm
 - iii. Limit
 - iv. None of the above
- 3 Holding Contact is also known as _____.
 - i. Sealing Contact
 - ii. Latching Contact
 - iii. Both i) and ii)
 - iv. None of the above
- 4 PLC Consists of _____.
 - i. Input Module
 - ii. Output Module
 - iii. Programming Device
 - iv. All of the above
- 5 _____ Switch activates when pressed, but remains activated when it is released.
 - i. Momentary Pushbutton
 - ii. Flush Pushbutton
 - iii. Both i) and ii)
 - iv. None of the above
- 6 Holding down the _____ button will not cause the machine to RUN more than one cycle.
 - i. ON
 - ii. RUN
 - iii. CYCLE
 - iv. None of the above
- 7 Scan time is typically measured in milliseconds and is related to the _____.
 - i. Speed of CPU
 - ii. Length of the ladder diagram
 - iii. Types of instructions in the program
 - iv. All of the above
- 8 Disagreement Circuit is basically _____ operation.
 - i. AND
 - ii. NOR
 - iii. XNOR
 - iv. None of the above
- 9 Guarded Pushbuttons are used in application/s such as _____.
 - i. START
 - ii. CYCLE
 - iii. JOG
 - iv. All of the above
- 10 _____: the state in which the machine is ON but not RUNNING.
 - i. CYCLE
 - ii. RUN
 - iii. JOG
 - iv. None of the above

Conti...

Que 2 Short Questions (Attempt any TEN)

[20]

- 1 Describe I/O Update.
- 2 What do you mean by Limit Switch?
- 3 Explain Two - Handed RUN Actuation.
- 4 Explain Disagreement Circuit.
- 5 Differentiate between Momentary Pushbutton and Maintained Pushbutton.
- 6 What do you mean by Output Image Register?
- 7 What is JOG (condition in PLC)?
- 8 What is Selector Switch?
- 9 What do you mean by Program Components?
- 10 Draw the ladder logic rung for a normally open IN_1 AND'ed with a normally closed IN_2 driving a coil CR_1 .
- 11 Define Scan Cycle.
- 12 Explain AND OR Logic.

Que 3 [A] With necessary Timing Diagram and Schematic Symbols, explain Delay - On Timer (TON) Relay. **[05]**

[B] Write a note on Pushbutton Switch Actuators. **[05]**

OR

[C] With necessary Timing Diagram and Schematic Symbols, explain Delay - Off Timer (TOF) Relay. **[05]**

[D] Give an account of Contactor. **[05]**

Que 4 [A] Discuss Ground Test with necessary Circuit. **[05]**

[B] Give an account of Sealing Contacts. **[05]**

OR

[C] Write a note on Reference Designators. **[05]**

[D] Write a note on Anti - Tie Down and Anti - Repeat. **[05]**

Que 5 [A] Write a note on Solve the Ladder. **[10]**

OR

[B] Describe the PLC Configurations in length. **[10]**

Que 6 [A] Discuss Always - ON and Always - OFF Contacts. **[05]**

[B] Write a note on Oscillator (with respect to PLC). **[05]**

OR

[C] Give an account of Internal Relay. **[05]**

[D] Explain Majority Circuit. **[05]**
