

[42]

SARDAR PATEL UNIVERSITY**B.Sc. Semester V (Electronics & Communication) Examination****Date & Day: 11th November 2019, Monday****Time: 10:00 AM to 01:00 PM****Subject Code: US05CELC01****Subject: Analog Circuit Design & it's Applications****Total Marks: 70***Note : The figure right indicates full marks***Q-1 Multiple Choice Questions.****[10]**

1. _____ coupling is generally employed in power amplifiers
[a] Transformer [b] RC
[c] Direct [d] None
2. The 555 timer IC is used for _____
[a] Time delay [b] Rectification
[c] Amplification [d] All of above
3. The efficiency of a Class A amplifier is _____
[a] 25-50% [b] 50%
[c] 78.5 [d] Above 78.5%
4. An oscillator employs _____ feedback
[a] Negative [b] Positive
[c] Both (a) & (b) [d] None
5. If the output of an amplifier is 10 V and 100 mV from the output is fed back to the input, then feedback fraction is _____
[a] 10 [b] 1
[c] 0.1 [d] 100
6. Bistable multivibrator has _____ stable states.
[a] 2 [b] 1
[c] 0 [d] 3
7. In a _____ amplifier, the current flows only during positive half cycle.
[a] Class A [b] Class B
[c] Class AB [d] Class C
8. _____ oscillator employs two inductor in series & capacitor in parallel.
[a] Hartley [b] RC phase shift
[c] Collpitt's [d] None
9. A class A power amplifier uses _____ transistor
[a] 3 [b] 1
[c] 4 [d] 2
10. Negative feedback in an amplifier _____
[a] Increases noise [b] Reduces bandwidth
[c] Reduces gain [d] Increases frequency

Q-2 Answer the following (Any Ten) questions.**[20]**

1. Why feedback is necessary in amplifier?
2. List out the different types of multivibrators.
3. Define: oscillator.

P.T.O

- 4 Differentiate between negative and positive feedback.
- 5 List out the applications of crystal oscillator.
- 6 Draw the labeled circuit of a collpitt's oscillator.
- 7 Draw a circuit diagram of pulse position modulation.
- 8 Write a note on Class AB amplifier.
- 9 List out the different types of feedback in amplifier.
- 10 Define : Multivibrator .
- 11 Explain the miller's theorem..
- 12 Note down the application of 555 timer Ic.

- Q-3 A. What is power amplifier? Explain in detail about transformer coupled class A amplifier. [07]
- B. Differentiate between Class A and Class B amplifier. [03]

OR

- Q-3 With necessary circuit diagram show that maximum efficiency achievable in Class B push pull amplifier is 78.5%. [10]
- Q-4 A. With the help of necessary diagram explain the concept of feedback of an amplifier. [06]
- B. Calculate the gain of a negative feedback amplifier with an internal gain $A=100$ and feedback factor $\beta=1/10$. [04]

OR

- Q-4 Define: Negative feedback. Derive the expression for negative feedback of an amplifier using voltage series feedback circuit. [10]
- Q-5 A. What is piezoelectric effect? Explain in detail crystal oscillator. [05]
- B. Explain Hartley oscillator. [05]

OR

- Q-5 A. Give the meaning of terms: (a) damping oscillation (b) growing oscillation and (c) Sustained oscillation. [05]
- B. Note down the principle of RC network and explain the RC phase shift oscillator. [05]
- Q-6 Sketch the pin diagram of 555 timer Ic also explain each of its pin in brief. [10]

OR

- Q-6 Define: astable multivibrator. Explain the astable multivibrator with it circuit diagram also draw the functional diagram [10]