No. of Printed Pages: 02

SARDAR PATEL UNIVERSITY

B.Sc. (5th Semester) Examination Friday, 22nd November 2019 10:00 a.m. to 1:00 p.m.

US05CELE06 – Analog Communication

Total Marks: 70

Q.1	Choose the correct answer [10]
1.	Quality of the reproduced sound program depends on	
	(a) Fidelity (b) Adaptability of the receiver (c) Sensitivity of receiver	
2.	A Radio receiver the RF carrier to get back the original modulation frequency	
	voltage.	
	(a) Amplifies (b) Accepts (c) Detects	
3.	reproduces the sound to produce the original programs.	
	(a) Loudspeaker (b) Receiver (c) Oscillator	
4.	A properly designed AVC system reduces thevariation due to fading from a hig	h
	value of 30 to 40 dB to a power small value of 3 to 4 dB.	
	(a) Current (b) Amplitude (c) Power	
5.	per stage of I.F. amplifier is higher than that in one stage of RF amplifier using t	ne
	same transistor.	
	(a) Current (b) Amplification (c) Voltage	
6.	Electron multiplier system consisting of succession of surfaces called which are	
	kept at progressively higher positive potential and treated to produce secondary electron	
	emission.	
	(a) Anodes (b) Cathodes (c) Dynodes	
7.	The Aspect ratio in TV communication is always adjusted to	
	(a) 4:3 (b) 3:4 (c) 16:9	
8.	The signals of the desired channel in TV receivers are selected by	
	(a) RF tuner (b) Balun (c) IN traps	
9,	The device used to match the impedance at the TV receiver input is called	
	(a) Balun (b) IF traps (c) RF tuner	
10.	The RF tuner through the use of isolates the local oscillator from the antenna.	
	(a) RF Amplifier (b) AF Amplifier (c) Frequency mixer	
Q.2		20]
1.	What is a radio receivers?	
2.	What are the functions of RF amplifier used in a radio receiver?	
3.	Give classifications of radio receiver.	
4.	What is the need of delayed AGC ?	
5.	Why local oscillator and RF amplifier are ganged together?	
6.	Draw the circuit of linear diode detector with \mathbb{I} -filter and simple AVC.	
	What is Aspect ratio?	
Ø	What is the function of television cameras tube?	P 1

9. What is limitation of rectangular switching? 10. What are the function of RF amplifier used in TV receiver? 11. What is the function of IF Traps in the TV receiver? 12. What are the basic requirements of video IF amplifier used in TV receiver? Q.3 Draw the block diagram of super heterodyne receiver and briefly explain the function of the [10] different constituent parts. OR Q.3 List the basic functions of AM receiver and explain each in detail. [10] Q.4 Draw the circuit of RF amplifier used in a radio receiver and explain its working. [10] OR Q.4 Draw the circuit of frequency mixer using two transistors used in broadcast radio receiver & [10] explain its working. [10] Q.5 Explain the construction and working of image orthicon. OR [10] Q.5 Discuss in detail the composite video signal. [10] Q.6 Discuss in detail the interstage coupling methods. [10] Q.6 Draw the block diagram of broadcast TV receiver and explain it.