

- 1 Explain importance of 'two-handed operation' of programmable logic controller (PLC).
 - 2 What do you mean by 'JOG' and 'ON' with respect to programmable logic controller (PLC)?
 - 3 What is pushbutton? Explain it with respect to programmable logic controller (PLC).
 - 4 Explain terminology 'RUN' and 'CYCLE' in terms of programmable logic controller (PLC).
 - 5 Why output module is used in programmable logic controller (PLC)?
 - 6 Enlist different programmable logic controller (PLC) programming languages.
 - 7 What is control system?
 - 8 In terms of programmable logic controller (PLC), explain what oscillator is.
 - 9 Explain what internal relay is. Is it programmable component?
 - 10 Draw programmable logic controller (PLC) ladder diagram of disagreement circuit.
 - 11 Discuss importance of fuse with respect to industrial control systems.
 - 12 Why indicator lamps are used in industry?
- Que 3 [A] Why 'control transformers' are used in industrial control systems? [05]
 [B] Explain why delay-on and delay-off timer relays are used in advanced control systems? [05]
- OR
- Que 3 [A] With necessary symbol/s, explain 'selector switch' used in industrial automation. [05]
 What do you mean by 'pushbutton switch actuator'?
- [B] Write a note on electromechanical relay. What is its use? [05]
- Que 4 [A] Why latching contacts are used in programmable logic controller (PLC)? [05]
 [B] Draw programmable logic controller (PLC) ladder diagram of OR AND operation. [05]
 Explain it.
- OR
- Que 4 Give an account of 'single cycle' with respect to programmable logic controller (PLC). [10]
- Que 5 [A] Give programmable logic controller (PLC) configuration. Explain it in detail. [05]
 [B] What is programmable logic controller (PLC)? How it differs from personal computer (PC)? [05]
- OR
- Que 5 With respect to industrial automation and programmable logic controller (PLC), explain what 'solve the ladder' is. [10]
- Que 6 [A] Draw the programmable logic controller (PLC) ladder diagram of majority circuit. [05]
 Explain it.
- [B] Draw the programmable logic controller ladder diagram of 'always-ON' and 'always-OFF' contacts. Explain them. [05]
- OR
- Que 6 [A] Write a note on physical components of programmable logic controller (PLC). [05]
 [B] What is 'program component'? Explain it in detail with respect to programmable logic controller (PLC). [05]