

[30]

**SARDAR PATEL UNIVERSITY**

B.Sc. (V<sup>th</sup> SEM.) ELECTRONICS  
 1<sup>st</sup> NOVEMBER-2018 EXAMINATION  
 SUB. - INDUSTRIAL ELECTRONICS- I  
 SUB.CODE-US05CELE05

MARKS-70

TIME:-10:00 am to 1:00 pm

[10]

**Q-1 Choose correct answer**

1. \_\_\_\_\_ Connection of SCR used for controlling very high current.  
 (A) series (C) bi-directional  
 (B) parallel (D) None of above
2. UJT mainly used for \_\_\_\_\_.  
 (A) relaxation oscillator (C) amplification  
 (B) rectification (D) None of above
3. Thyristor mainly used for \_\_\_\_\_.  
 (A) Rectification (C) Relaxation oscillation  
 (B) control power (D) None of above
4. Recommended method to TURN-ON SCR is \_\_\_\_\_.  
 (A) Triggering by A.C signal (C) Triggering by D.C signal  
 (B) Triggering by pulse signal (D) None of above
5. SCS means \_\_\_\_\_.  
 (A) silicon unilateral switch (C) silicon port switch  
 (B) silicon uni-junction switch (D) None of above
6. Static equalising circuit is compensating circuit to produce uniform voltage in \_\_\_\_\_ operation of SCR.  
 (A) parallel (C) normal  
 (B) series (D) None of above
7. TRIAC \_\_\_\_\_ type of device.  
 (A) multi-directional (C) bi-directional  
 (B) uni-directional (D) None of above
8. \_\_\_\_\_ Connection of SCR used for controlling very high voltage.  
 (A) series (C) bi-directional  
 (B) parallel (D) None of above
9. \_\_\_\_\_ is a circuit which convert DC power in to AC power at desired output voltage.  
 (A) Rectifier (C) Filter  
 (B) Inverter (D) None of above
10. Dc motor consists of \_\_\_\_\_.  
 (A) SCR (C) Oscillator  
 (B) Stator (D) None of above

[20]

**Q-2 Short answer type question. (any ten)**

- 1 Define string efficiency.
- 2 State function of gate in SCR.
- 3 Differentiate between semiconductor and thyristor device.
- 4 Differentiate between D.C. motor and stepper motor.
- 5 Define reverse recovery current  $I_{RR}$ .
- 6 List application of thyristor device.
- 7 Differentiate TRIAC and SCR.
- 8 State different type of inverter circuit.
- 9 State principle of operation of stepper motor.
- 10 Draw symbol of TRIAC and DIAC.
- 11 Define phase angle.
12. What do you mean by relaxation oscillator.

[P.T.O.]

- Q.3 List the thyristor family components and Discuss principle of operation and characteristics of SCR. [10]
- OR
- Q.3(A) Discuss different method of turning on a SCR with TURN-ON characteristics. [06]
- Q.3(B) Briefly discuss TURN OFF mechanism of SCR. [04]
- Q.4 Describe the series operation of SCR with necessary diagram and compensation circuits. [10]
- OR
- Q.4 Explain the parallel operation of SCR with necessary diagram and compensation circuits. [10]
- 
- Q.5(A) Discuss characteristics and operation of UJT with necessary diagram. [06]
- Q.5(B) Briefly explain UJT as a relaxation oscillator. [04]
- OR
- Q.5(A) Discuss use of SCR as static AC circuit breaker. [05]
- Q.5(B) Explain different triggering mode of TRIAC with necessary diagram. [05]
- Q.6(A) Explain parallel inverter giving necessary diagram and waveforms. [06]
- Q.6(B) Write a short note on stepper motor [04]
- OR
- Q.6 Draw the schematic diagram of D.C motor and discuss its working in detail. [10]

— X —