

[22/23]

SEAT No. \_\_\_\_\_

Total printed Pages:02

**SARDAR PATEL UNIVERSITY**

**F.Y.B.Sc(CA & IT) –1<sup>st</sup>SEM Examination- 2019**

**US01CIIT23: Computer Organization & Digital Electronics**

Date: 21/11/2019, Thursday

Time : 10:00 A.M to 01:00 P.M

Total Marks 70

[10]

**Q1 Multiple Choice Question**

- 1 Computer hardware refers to the \_\_\_\_\_ parts of a computer.  
A) Logical B) Physical C) Data D) None of above
- 2 Which of the following is not an input unit?  
A) Printer B)Scanner C)Keyboard D) None of above
- 3 \_\_\_\_\_ is a permanent memory.  
A) EPROM B) EEPROM C) RAM D) ROM
- 4 The Digital system usually operates on \_\_\_\_\_ system  
A) Binary B) Decimal C) Octal D) Hexadecimal
- 5 The number 178 is equivalent to \_\_\_\_\_ binary.  
A) 111 B) 110 C) 1000 D) 1111
- 6 In Hexadecimal number system F stands for \_\_\_\_\_  
A) 15 B) 14 C) 16 D) 12
- 7 Half adder consists of \_\_\_\_\_ & \_\_\_\_\_ gates.  
A) XOR,OR B) XOR,AND C) XNOR, AND D) XNOR, OR
- 8 An invert gate is also known as \_\_\_\_\_ gate.  
A) NOR B) NOT C) XNOR D) NAND
- 9 A multiplexer is also called a \_\_\_\_\_  
A) Data Multiplier B) Data Selector  
C) Data Inverter D) Data Remover
- 10 \_\_\_\_\_ is a memory element that stores binary digit.  
A) Binary Adder B) Decoder C) Multiplexer D) Flip-flop

[20]

**Q2 Short Questions (Attempt any Ten)**

- 1 Define the term 'Hardware' and 'Software'.
- 2 What is secondary storage?
- 3 Give the Full Form 'EEPROM' and 'SSDD'
- 4 What is 3-bits grouping conversion method?
- 5 What is number system? List out various numbersystems.
- 6 Explain the conversion of decimal to Octal method.
- 7 Explain NAND, OR Gate.
- 8 Explain Associative Law.
- 9 Explain half adder in detail.
- 10 Define encoder in short.
- 11 Explain D Flip-flop.
- 12 What is negative clocking?

(P.T.O)

Q3

- A Explain Transfer rate [05]
- B Explain Printers in detail. [05]

OR

- A Draw a block diagram of basic organization of a computer system and explain the functions of the various units. [03]
- B List various applications of computer. [07]

Q4

- A Explain the conversion of Binary to Decimal with suitable example. [05]
- B Explain binary addition with suitable examples. [05]

OR

- A Explain Hexadecimal to Decimal with suitable examples. [05]
- B Explain binary subtraction with suitable examples. [05]

Q5

- A Prove that  $ABC' + ABC = AB$  using truth table. [05]
- B Explain XOR, AND, NOR gate. [05]

OR

- A Explain AND, NOR, NOT gate. [05]
- B Explain de Morgan's first and second theorem. [05]

Q6

- A Explain RS flip-flop with NOR Latches and NAND Latches. [10]
- A Explain 8 x 3 line encoder and 4 x 1 demultiplexer in detail. [10]

— X —  
②