

[127/A21]
GUT

DATE No. _____

No. of Printed Pages : 2

સરદાર પટેલ યુનિવર્સિટી

બી.એસ.સી.પરીક્ષા: સેમેસ્ટર-1

વિષય: ફિઝિક્સ

કોર્સ: US01CPHY02

પેપર: જગતતત્ત્વ વિશ્લેષણ, પ્રકાશશાસ્ત્ર અને લેસર

તા. 25-10-2018 (ગુરુવાર)

સમય: બપોરના 2.00 થી 4.00

કુલ માર્ક: 70

જોધું: (1) સંજાથો તેમના પ્રચલિત અર્થમાં છે.

(2) જમણી બાજુ દર્શાવેલ આંક પ્રક્રણના ગુણ દર્શાવે છે.

Q.1 બહુ વૈકલ્પિક પ્રશ્નો: (બધા પ્રશ્નો ફરજિયાત છે, દરેક પ્રક્રણનો 1 માર્ક છે) 10

1. $j = 3$ અને $b = 6$ ધરાવતા જગતતત્ત્વમાં સ્વતંત્ર નોડ સમીકરણોની સંખ્યા _____ હોય.

(a) 2 (b) 3 (c) 9 (d) 18

2. સમાંતર જોડણમાં રહેતા બે અવરોધો માટે _____ નું મૂલ્ય જુદું હોય છે.

(a) વોલ્ટેજ (b) આવૃત્તિ (c) વિધુતપ્રવાહ (d) કંપવિસ્તાર

3. _____ એ લુપનું સૌથી નાનામાં નાનું રૂપ છે કે જેને વધુ આગળ વિલાઘત કરી શકાતું નથી.

(a) શામા (b) લૂપ (c) વૃક્ષ (d) જાળી

4. વિન બ્રિજ વડે _____ નું અણાત મૂલ્ય શોધી શકાય છે.

(a) અવરોધ (b) ઇન્ડકટન્સ (c) આવૃત્તિ (d) કેપેસીટન્સ

5. મેક્સવેલ બ્રિજ માટે Q નું યોગ્ય મૂલ્ય _____ છે.

(a) $1 < Q < 10$ (b) $0.1 < Q < 10$ (c) $1 < Q < 100$ (d) $Q > 10$

6. કેપેસીટર dc પ્રવાહને _____ અવરોધ પુરો પાડે છે.

(a) થૂન્ય (b) અનંત (c) ઓછો (d) નહિયત

7. _____ એ પ્રકાશીય ઘટના નથી.

(a) ધૂલીકરણ (b) ગુરુત્વાકર્ષણ (c) વ્યતિકરણ (d) વડીભવન

8. માઇક્રોન ઇન્ટરફેરોમીટરમાં સમકેન્દ્રીય વર્તુળાકાર શલાકાઓ મેળવવા માટે પ્રતિબિંબ M_1' અને M_2' ના સ્થાન _____ હોવા જોઈએ.

(a) સમાંતર (b) વ્યસ્ત (c) સંપાત (d) પરસ્પર લંબ

9. _____ એ લેસરનો ગુણધર્મ છે.

(a) ઓછી તીવ્રતા (b) વધુ સુસંબંધિતા (c) ભૂમિતતા (d) અલ્પ દિશાપણું

10. B_{21} ને આઇનસ્ટાઇનનો _____ ઉત્સર્જન ગુણાંક (emission coefficient) કહે છે.

(a) સ્વયં (spontaneous) (b) પરમાણ (c) થૂન્ય (d) પ્રેરિત (stimulated)

Q.2 કોઈ પણ દસ પ્રશ્નોના દ્રકમાં જવાબ લખો: (દરેક પ્રક્રણના 2 માર્ક છે) 20

1. થેવેનિન પ્રમેયનું વિધાન લખો.

2. વ્યાખ્યાયિત કરો: મધ્યવર્તી (node) અને જક્કશન.

①

(૧૮૦)

3. જગતંત્ર માટે વંધગાળા (લૂપ) અને જાળી (મેશ) વચ્ચેનો લેદ વ્યાખ્યાયિત કરો.
4. શેરિંગ બ્રિજનો સંશાત્મક પરીપથ દોરો.
5. મેક્સવેલ બ્રિજની મર્યાદાઓ લખો.
6. 2C બ્રિજના સંતુલન માટેની બે શરતો લખો.
7. માઇકલ્સન ઇન્ટરફેરોમીટરની વ્યવહારિક ઉપયોગિતાઓ લખો.
8. રેલેનું વિલેદન પ્રમાણ આફુતિસહ દ્રોકમાં સમજાવો.
9. ટેલિસ્કોપ, માઇકોસ્કોપ, પિઝમ, ગ્રેટિંગની વિલેદનશક્તિ માટેના માત્ર સુત્રો લખો.
10. આફુતિસહ દ્રોકમાં સમજાવો: સ્વચ્ય (spontaneous) અને પ્રેરિત (stimulated) ઉત્સર્જન.
11. દ્રોકનોંધ લખો: પોથ્યુલેશન ઇન્વર્જન.
12. તબીબી ક્ષેત્રમાં લેસરની ચાર વ્યવહારિક ઉપયોગિતાઓ લખો.

- પ્ર.3 (a) બે જાળીવાળા જગતંત્રનો પરીપથ દોરી તેનું વિશ્લેષણ કરી જરૂરી જાળી-સમીકરણો મેળવો. 06
(b) વોલ્ટેજ લાજડ પ્રમેયનું વિધાન લખો અને સાબિત કરો. 04

અથવા

- પ્ર.3 (a) એક નોડ જોડીવાળા જગતંત્રનો પરીપથ દોરી તેનું વિશ્લેષણ કરી જરૂરી નોડ-સમીકરણ મેળવો. 06
(b) સંપાતપણાના પ્રમેયનું વિધાન લખો અને સાબિત કરો. 04

- પ્ર.4 (a) લિસ્ટનાભ્રિજ પરીપથનો થેવેનિન સમતૂલ્ય પરીપથ મેળવી I_g નું સમીકરણ તારવો. 06
(b) લિસ્ટનાભ્રિજ પરીપથની મર્યાદાઓ લખો. 04

અથવા

- પ્ર.4 (a) મેક્સવેલ બ્રિજ પરીપથ વડે ગુંચળાનું અજાત ઇન્ડકટન્સ શોધવા માટેનું જરૂરી સમીકરણ તારવો. 06
(b) જરૂરી વિધુતપરીપથ દોરી d.c. બ્રિજના સંતુલન માટેની શરત મેળવો. 04

- પ્ર.5 (a) માઇકલ્સન ઇન્ટરફેરોમીટરનો સિધ્યાંત, રચના, કાર્ય વર્ણની તેના ઉપયોગો લખો. 06
(b) માઇકલ્સન ઇન્ટરફેરોમીટરમાં ચલિત અરીસાને 3×10^{-5} m ખ્રેડતાં પ્રદિક્ષેત્રમાં છેદક તાર પાસેથી કેટલી શાલાકાઓ પસાર થશે? $\lambda = 6000 \text{ \AA}$ લો. 04

અથવા

- પ્ર.5 (a) જરૂરી આફુતિ દોરી ટેલિસ્કોપની વિલેદનશક્તિ માટેનું સુત્ર મેળવો. 06
(b) અલગ પારખી શકાય તેવા બે તારાઓ વચ્ચેનું, ટેલિસ્કોપના D વ્યાસ ધરાવતા વસ્તુશાચ વડે મપાતું કોણીય વિલાજન 4.85×10^{-6} રેડિયન છે તો D નું મૂલ્ય શોધો. $\lambda = 6000 \text{ \AA}$ લો. 04

- પ્ર.6 જરૂરી આફુતિઓ દોરી CO₂ લેસર સમજાવો. તેની વિવિધ ખાસિયતો કઈ છે તે જણાવો. 10

અથવા

- પ્ર.6 Nd:YAG ની રચના, કાર્યપદ્ધતિનું વર્ણન કરો. તેની વિવિધ ખાસિયતો કઈ છે તે જણાવો. 10

—X—
(2)

[127/A21]
Eng

Seat No. _____

No. of Printed Pages : 2

SARDAR PATEL UNIVERSITY

B.Sc. Examination (Semester - 1)

Subject: Physics Course: US01CPHY02 Title: Network Analysis, Optics and Laser

Date: 25-10-2018 (Thursday)

Time: 02.00 P.M. TO 04.00 P.M.

Total Marks: 70

Note: (i) All the symbols have their usual meanings.

(ii) Figure at the right side of question indicates full marks.

Q-1 Multiple Choice Questions (Attempt All: Each of 1 mark) 10

- (1) In a network with $j=3$ and $b=6$, number of independent node equations is _____.
(a) 2 (b) 3 (c) 9 (d) 18
- (2) For two resistors connected in parallel, flowing of _____ will be different.
(a) voltage (b) frequency (c) current (d) amplitude
- (3) _____ is the most elementary form of the loop which cannot be further divided.
(a) branch (b) loop (c) tree (d) mesh
- (4) Wien bridge is used to measure unknown _____.
(a) resistance (b) inductance (c) frequency (d) capacitance
- (5) Maxwell bridge is suitable for Q in the range _____.
(a) $1 < Q < 10$ (b) $0.1 < Q < 10$ (c) $1 < Q < 100$ (d) $Q > 10$
- (6) Capacitor offers _____ resistance to dc current.
(a) zero (b) infinite (c) low (d) very low
- (7) _____ is not an optical process.
(a) polarization (b) gravitation (c) interference (d) refraction
- (8) Circular fringes obtains in Michelson interferometer if images M_1 and M_2 are _____.
(a) parallel (b) crossed (c) overlapping (d) perpendicular
- (9) _____ is one of the properties of a LASER.
(a) low intensity (b) highest coherence (c) illusion (d) low directionality
- (10) B_{21} is the Einstein's coefficient for _____ emission of radiation.
(a) spontaneous (b) pumping (c) zero (d) stimulated

Q-2 Answer any TEN in short (Each of 2 marks) 20

- (1) Give the statement of Thevenin's theorem.
- (2) Define node and junction.
- (3) Differentiate between loop and mesh of a network.
- (4) Draw the labeled circuit of a Schering bridge.
- (5) Enlist the limitations of a Maxwell bridge.
- (6) Write two conditions for balancing of ac bridge.

- (7) Write the applications of Michelson interferometer.
- (8) Along with the figure explain Rayleigh's criterion for resolution.
- (9) Write the formula only for resolving power of Telescope, Microscope, Prism, grating.
- (10) Explain with diagram: spontaneous emission and stimulated emission.
- (11) Write a short note on population inversion.
- (12) State four applications of LASER in field of medical science.

- Q-3** (a) Draw two mesh network and obtain necessary mesh equations for its analysis. **06**
 (b) Write statement and explain voltage divider theorem. **04**

OR

- Q-3** (a) Draw one node pair network and obtain necessary node equation for its analysis. **06**
 (b) Write statement and explain superposition theorem. **04**
Q-4 (a) Obtain Thevenin equivalent circuit of a wheatstone bridge. Derive expression for I_g . **06**
 (b) Enlist the limitations of a Wheatstone bridge. **04**

OR

- Q-4** (a) Derive the equation to find out value of unknown inductance by Maxwell bridge. **06**
 (b) Derive balance condition for dc bridge. **04**
Q-5 (a) Write the principle, construction, working and uses of Michelson interferometer. **06**
 (b) When the movable mirror of Michelson interferometer moved a distance of 3×10^{-5} m,
 how many fringes will be displaced? Take $\lambda = 6000 \text{ \AA}$. **04**

OR

- Q-5** (a) Giving neat diagram derive the equation for resolving power of a telescope. **06**
 (b) Two distant stars subtend an angle of 4.85×10^{-6} radian at the objective of telescope.
 Find out the diameter of the objective required to resolve stars. Take $\lambda = 6000 \text{ \AA}$. **04**
Q-6 Write a note on CO₂ laser. Discuss its various features. **10**

OR

- Q-6** Write a note on Nd:YAG laser. Discuss its various features. **10**

—X—

(2)