

[25 / A-56]

SC
No. Of Printed Pages: 2

SARDAR PATEL UNIVERSITY
S.Y.B.Sc Fourth Semester Examination, (under CBCS)
USO4CINS01

(Signal conditioning system)

Wednesday, 6th April 2016

10.30 AM - 01.30 PM

Marks: 70

[10]

Q.1 Multiple choice questions.

- (1) In electronic aided measurement first stage is_____.
(a) Transducer (b) Recorder
(c) Amplifier (d) None of above
- (2) The main problem of a DC amplifier is_____.
(a) Voltage (b) Filtering
(c) Frequency (d) Drift
- (3) Operational amplifier gain range is_____.
(a) $10^{-10} - 10^2$ (b) $10^{-10} - 10^2$
(c) $10^4 - 10^8$ (d) $10^9 - 10^{18}$
- (4) Light intensity meter is calibrated in terms of _____.
(a) Lumen (b) pressure
(c) Temperature (d) None of above
- (5) In thermistor temperature increase when resistance is _____.
(a) Increase (b) Decrease
(c) Low (d) High
- (6) Simple bridge consists of _____ arm.
(a) Two (b) Three
(c) Five (d) Four
- (7) Maxwell's bridge Quality factor range is_____.
(a) 1-3 (b) 1-4
(c) 1-10 (d) 1-5
- (8) A DAC is usually an _____ part of any DAC.
(a) Integral (b) Derivative
(c) Analog (d) None of above
- (9) Step size is the size of the jump in the _____ wave form.
(a) Linear (b) Staircase
(c) Square (d) Non-linear
- (10) The counter type ADC is also known as _____ ADC.
(a) Digital ramp (b) Analog ramp
(c) (a) & (b) (d) None of above

Q.2 Short answer type questions (Attempt any ten)

[20]

- (1) Enlist the characteristic of Op-amp.
- (2) Draw the equivalent circuit of op-amp and write the equation.

- (3) What is chopper? Draw the circuit of chopper type DC amplifier.
- (4) Draw the diagram of solid state modulator and demodulator.
- (5) Draw the circuit of Wheatstone's bridge. And find the unknown resistance, where $R_1 = 10K$, $R_2 = 5K$, $R_3 = 60K$
- (6) Draw the block diagram of interfacing of a digital computer to the analog world.
- (7) Draw the Maxwell bridge circuit and find the unknown inductance where $R_1 = 470K$, $R_2 = 150K$, $R_3 = 5.1K$ and $C_1 = 0.01\mu f$.
- (8) Write about voltage to frequency converter
- (9) Draw the pin diagram of the ADC 0801
- (10) Draw the block diagram of an instrumentation system and explain it.
- (11) Determine the resolution of (a) 8-bit DAC and (b) 12-bit DAC in terms of percentage.
- (12) Write about bipolar DACs.

- Q.3 A Write a detail note on differentiation amplifier [6]
 B Discuss about inverting amplifier. [4]

OR

- Q.3 A Draw the circuit of integrator and explain in detail [6]
 B Write a note on non-inverting amplifier [4]

- Q.4 A Write a detail note on diode bridge modulator. [5]
 B Write about analog weight scale [5]

OR

- Q.4 A Draw the necessary circuit of synchronous modulator/demodulator and explain it. [5]
 B Write about transistor choppers in detail. [5]

- Q.5 A Draw the circuit of kelvin's double bridge and find the equation for unknown resistance. [6]
 B Give a detail note on Schering's bridge. [4]

OR

- Q.5 A Draw the circuit of Hay's bridge and explain in detail. [6]
 B Give a detail note on wheatstone's bridge. [4]

- Q.6 A Write about R-2R ladder type DAC and explain any two cases with necessary diagram. [6]
 B Write a brief note on flash type ADC. [4]

OR

- Q.6 A Explain counter type ADC with diagram. [6]
 B Write a note on weighted resistor type DAC. [4]

X = XEX

(2)