

SC

**SARDAR PATEL UNIVERSITY**  
**S.Y.B.Sc IV<sup>th</sup> Semester Examination, (under CBCS)**  
**USO4CINS01**  
**(Signal Conditioning Systems)**  
**Saturday, (7<sup>th</sup> April 2018)**  
**10.00 am to 01.00 pm.**

MARK :70

- Q.1 Multiple choice questions. [10]**
- (1) The simplest type of ADC is \_\_\_\_\_ type.  
(a) counter (b) flash (c) successive (d) dual slope
  - (2) The degree of clones to the true value of the quantity under measurement is called \_\_\_\_\_.  
(a) Error (b) Accuracy (c) Precession (d) Mean
  - (3) Maxwell's bridge quality factor range is \_\_\_\_\_.  
(a) 1-3 (b) 1-4 (c) 1-10 (d) 1-5
  - (4) The gain of the Op- Amp is \_\_\_\_\_.  
(a) zero (b) infinite (c) high (d) low
  - (5) \_\_\_\_\_ bridge is used to measure high factor Q values.  
(a) Maxwell's (b) Kelvin (c) Wein (d) Wheatsone
  - (6) The Wagner's ground is used to measure \_\_\_\_\_.  
(a) capacitive (b) resistive (c) inductive (d) stray capacitances
  - (7) The simple bridge consists of \_\_\_\_\_ arms.  
(a) two (b) three (c) four (d) five
  - (8) The most reliable substitutes for electromechanical chopper are \_\_\_\_\_.  
(a) diode bridge modulator (b) transistor chopper  
(c) both (a)& (b) (d) none of above
  - (9) The counter type ADC is also known as \_\_\_\_\_ ADC.  
(a) digital ramp (b) analog ramp (c) both (a)&(b) (d) none of above
  - (10) The signal conditioner receives the signal from \_\_\_\_\_.  
(a) power supply (b) amplifier (c) transducer (d) oscillator

- Q.2 Short answer types question (Any Ten) [20]**
- (1) Difference between AC and DC bridge.
  - (2) Enlist limitations of Wheatstone bridge.
  - (3) Classify different types of errors.
  - (4) Enlist important features of an instrumentation amplifier.
  - (5) Enlist parameter of DAC.
  - (6) Draw a block diagram of typical OP AMP.
  - (7) Define: Modulator.
  - (8) A certain 12 bit BCD DAC has a full scale output of 19.98V. Determine converter step size.
  - (9) Explain in brief limiting errors.
  - (10) Draw the block diagram of 4 bit DAC using digital input.
  - (11) What are the precautions to be taken while using bridge?
  - (12) What is the need of A/D & D/A converters in controlling a process?
- Q.3 (a) Show a diagram and discuss the current to voltage converter. [6]**  
**(b) Write a short note on Op- Amp summing amplifier. [4]**
- OR**
- Q.3 (a) Discuss the non-inverting amplifier, also obtain an expression for the closed loop voltage gain of it. [6]**  
**(b) Write a short note on comparator using Op- Amp. [4]**
- Q.4 (a) What do you mean by significant figures? Giving suitable examples explain it. [6]**  
**(b) Define: Systematic error. [4]**
- OR**
- Q.4 (a) Explain the difference between accuracy & precision in detail. [6]**  
**(b) What do you mean by statical analysis? Discuss it [4]**
- Q.5 (a) Discuss the Maxwell bridge in detail. [6]**  
**(b) Write a short note on Hay bridge with necessary diagram. [4]**
- OR**
- Q.5 (a) Discuss the Wein bridge circuit and also give its diagram. [6]**  
**(b) Discuss the capacitance comparison bridge. [4]**
- Q.6 Write a note on counter type analog to digital converter. [10]**
- OR**
- Q.6 Explain successive approximation type ADC. [10]**