

[24]

SEAT No. _____

No. of Printed Pages : 02

SARDAR PATEL UNIVERSITY

B.Sc. (4th Semester) Examination

Tuesday, 9th April 2019

10:00 am to 01:00 pm

Electronics

US04CELE01- Electronics Devices and Applications

Total Marks : 70

Q.1 Multiple choice questions.

[10]

1. The JFET is a _____ controlled Device.
(a) Voltage (b) Current (c) Power
2. In a frequency response curve the output normally remains constant over the _____ range of frequencies.
(a) Low (b) Middle (c) High
3. _____ is the best FET biasing circuit.
(a) Potential Divider Bias (b) Self Bias (c) Fixed Voltage Bias
4. In Common Source Circuit the input and output signal are _____ phase with each other.
(a) 180° out of (b) 90° out of (c) 270° out of
5. In the symbol of enhancement mode MOSFET the line representing the channel is broken to indicate that channel does not exist until the _____ potential is applied.
(a) Gate (b) Drain (c) Source
6. The Common Drain amplifier is also Known as _____ follower.
(a) Drain (b) Gate (c) Source
7. The input impedance of Field Effect Transistor is _____.
(a) High (b) Low (c) Zero
8. The dynodes are electrodes which are treated to produce _____ emission.
(a) Neutron (b) Secondary (c) Primary
9. LEDs made from _____ emit infrared radiation.
(a) GaAs (b) GaAsP (c) GAP
10. The liquid crystal display is made from _____ compounds.
(a) Organic (b) Inorganic (c) Semiconductor

Q.2 Answer any TEN questions in brief

[20]

1. Why does the amplifier Gain falls at low Frequency?
2. Define Decibel.
3. List different FET parameters.
4. Draw the Symbols of depletion enhancement mode MOSFET.

(1)

(P.T.O)

5. Draw the potential divider circuit using P channel FET.
6. Draw the symbols of enhancement mode N-Channel MOSFET.
7. Draw the common drain ac equivalent circuit .
8. Draw the common source ac equivalent circuit .
9. Draw the ac equivalent circuit of common gate amplifier.
10. What does photoconductive cell consists of ?
11. What is Dynamic scattering ?
12. What is an LED ?

Q.3 Explain in detail the frequency response of an amplifier giving necessary figures. [10]

OR

- Q.3 [a] Explain the drain characteristics of N channel JFET with external bias. [06]
 [b] Discuss in detail the depletion region of N channel JFET. [04]

Q.4 Discuss in detail the enhancement mode MOSFET giving necessary figures. [10]

OR

Q.4 Discuss in detail the depletion enhancement MOSFET giving necessary figures. [10]

Q.5 Discuss in detail the working of common source amplifier giving necessary figures . [10]

OR

Q.5 Draw the circuit of common drain amplifier and explain its working in detail. [10]

Q.6 Discuss in detail the photo multiplier tube with the help of necessary diagrams. [10]

OR

Q.6 Discuss in detail the Liquid Crystal Display giving necessary diagrams. [10]

----- x -----