

26

SEAT No. _____

No. of Printed Pages: 2

SARDAR PATEL UNIVERSITY

B. Sc. Information Technology Examination, 4th Semester

Monday, 08th April, 2019

US04CINT01: Computer Organization & Digital Computer Electronic

Time: 10:00 AM to 01:00 PM

Total Marks: 70

Note: Answer of all the questions (including Multiple Choice Questions) should be written in the provided answer book only

Q:1 Give answers of following Multiple Choice Questions

[10]

- [01] In Octal Number system, base is _____
- (A) 2 (B) 8
(C) 10 (D) 16
- [02] In Hexadecimal Number system, F stands for _____
- (A) 13 (B) 14
(C) 15 (D) None of above
- [03] The output unit supplies the converted results to the
- (A) Outside world (B) Computer inside
(C) Hard Disk (D) None of above
- [04] _____ holds the instruction currently being executed.
- (A) Program Counter (B) Instruction Register
(C) Control Register (D) None of above
- [05] _____ is a collection of parallel wires for transmitting address, data and control signals.
- (A) Transmitter (B) Program Counter
(C) Bus (D) Control Unit
- [06] _____ is a register, which points to the next instruction to be fetched for execution.
- (A) Program Counter (B) Instruction Register
(C) Control Register (D) None of above
- [07] Invert gate has only _____ input and _____ output.
- (A) One, One (B) Two, One
(C) One, Two (D) Two, Two
- [08] De Morgan's first theorem says that a NOR gate is equivalent to _____
- (A) Bubbled OR (B) Bubbled AND
(C) Bubbled NOR (D) Bubbled NAND
- [09] In k-map, pair eliminates _____ variable(s) and their complements.
- (A) One (B) Two
(C) Three (D) Four
- [10] A flip-flop has _____.
- (A) One stable state (B) Two stable states
(C) No stable states (D) None of these

(D)

(P. T. O.)

- Q:2 Answer the following short questions (any Ten) [20]**
- [01] List the base of Binary, Octal and Hexadecimal number systems.
- [02] Explain the conversion of Decimal to Binary method.
- [03] Define the terms: Hardware, Software.
- [04] What is program counter?
- [05] What is instruction register?
- [06] What do you mean by processor-level parallelism?
- [07] What is logic gate? List all logic gates.
- [08] Explain NAND gate in detail.
- [09] Explain half adder.
- [10] Define encoder and decoder.
- [11] What is minterms?
- [12] Explain Sum of Product in detail.
- Q:3 [A] Draw a block diagram of Basic Organization of a Computer System [10] and explain the functions of the various units.**
- OR**
- Q:3 [B] Explain the conversion of Hexadecimal to Decimal with suitable [05] example.**
- [C] Explain the addition and subtraction of Binary with suitable [05] example.**
- Q:4 [A] Describe the Hamming code by giving an example. [05]**
- [B] Explain Pipelining detail. [05]**
- OR**
- Q:4 [C] Explain the internal organization of a typical Von – Neumann CPU. [05]**
- [D] Explain Array Computers in detail. [05]**
- Q:5 [A] Explain De' Morgan first and second theorem. [05]**
- [B] Explain Half – Adder with truth table and logic diagram. [05]**
- OR**
- Q:5 [C] Explain Associative law in detail. [05]**
- [D] What is Binary Adder? Explain in detail. [05]**
- Q:6 [A] What is Multiplexer? Explain 4 X 1 multiplexer in detail. [06]**
- [B] Explain K – Map for 3 variables with example. [04]**
- OR**
- Q:6 [C] Explain D Latches in detail. [06]**
- [D] Explain Comparator in detail. [04]**

