

(109)

SARDAR PATEL UNIVERSITY

Vallabh Vidyanagar - 388120

B.Sc. (2ND Sem) Examination - March/April 2018 [CBCS]Wednesday, 4th April, 2018

02:00 PM to 04:00 PM

US02CINV01 (Instrumentation - Vocational)

Basic Electronic Instruments

Maximum Marks: 70

Que 1 Each question below gives a multiple choice of answers. Choose the most [10] appropriate one.

- 1 A Train of Sine Waves which Contains 50 Positive Peaks and 50 Negative Peaks per Second has Frequency of ____ Hz.
 - a) 50×10^6
 - b) 50×10^3
 - c) 50
 - d) 50×10^{-6}
- 2 If the Phase Difference of Sinusoidal Wave is ____ Degree, the Wave is Considered as Out of Phase Signal.
 - a) 60
 - b) 90
 - c) 180
 - d) 270
- 3 According to Kirchoff's Current Law (KCL), the Algebraic Sum of Currents Meeting at a Junction is ____.
 - a) Zero
 - b) Very High and Positive
 - c) Very Low and Negative
 - d) Always One
- 4 An Ideal Constant Current Source has ____ Ohm Resistance.
 - a) Zero
 - b) One
 - c) Medium
 - d) Infinite
- 5 In Ideal Capacitive Circuit, Phase Difference Between Voltage and Current is ____ Degree.
 - a) 0
 - b) 90
 - c) 180
 - d) 270
- 6 Sharpness of Resonance is Ratio of ____ of the Circuit to Its Resonance Frequency.
 - a) Current
 - b) Voltage
 - c) Quality Factor
 - d) Bandwidth
- 7 Power Factor of Series Resonant Circuit is ____.
 - a) Zero
 - b) +1
 - c) -1
 - d) Infinite
- 8 Thevenin's Equivalent of a Circuit Consists of a Constant ____ Source and Equivalent Resistance in Series With It.
 - a) Current
 - b) Power
 - c) Voltage
 - d) Current and Voltage

(1)

(P.T.O.)

- 9 Inductive Reactance is ____.
- | | |
|----------------------------------------|--------------------------------------------------------|
| a) Proportional to Frequency | b) Inverseley Proportional to Frequency |
| c) Proportional to Square of Frequency | d) Inverseley Proportional to Square Root of Frequency |
- 10 Capacitive Reactance is ____.
- | | |
|--------------------------------------------------------|----------------------------------------|
| a) Inverseley Proportional to Square Root of Frequency | b) Proportional to Square of Frequency |
| c) Inverseley Proportional to Frequency | d) Proportional to Frequency |

Que 2 Short Questions (Attempt any TEN)

[20]

- 1 Explain What Network Circuit is.
- 2 Draw Only Waveform For Inductor Response to Sinusoidal Signals.
- 3 What Do You Mean By Peak to Peak Value In Terms of Sinusoidal Signal?
- 4 What is "Phase (Angle) Difference"?
- 5 Enlist Factors Which Determine the Energy Stored by Capacitor.
- 6 Briefly Explain KCL.
- 7 What Do You Mean By Phase Lagging and Phase Leading?
- 8 Write Briefly on Norton's Theorem.
- 9 Explain "Tuning RLC Circuit".
- 10 What is Resonance Circuit?
- 11 Explain What Quality Factor is.
- 12 Enlist Applications of Resonance Circuit.

Que 3 [A] Derive an Expression for the Average and Effective Values of the Sinusoidal Signals. Write on Form Factor. [05]

[B] Convert Following Polar Coordinates to Cartesian Coordinates, Vice Versa. [05]

- 1) $Z_T = 6 + j6$
- 2) $Z_T = 9 - j2$
- 3) $Z_T = 100 \angle 45^\circ$
- 4) $Z_T = 3 - j4$
- 5) $Z_T = 5 \angle 37^\circ$

OR

[C] Do As Directed: [05]


- 1) $j5 + (3 - j2)$
- 2) $(7 - j) - (6 + j2)$
- 3) $(9 + j2) + (1 + j)$
- 4) $(8 - j8) + (1 + j)$
- 5) $(5 - j2) + (j + 1)$

[D] Explain Following Terms With Respect to AC Signals With Necessary Figures: [05]

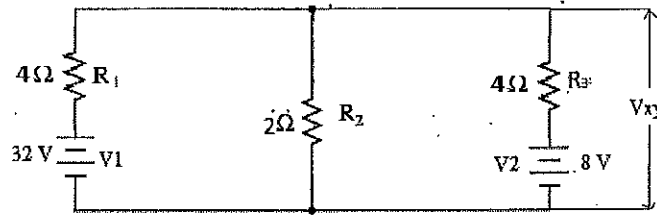- 1) Phase
- 2) Frequency
- 3) Periodic Time

Find Periodic Time of the Signal Produced By the Inverter With 10 KHz Frequency.

- Que 4 [A]** State Millman's Theorem. Determine The Value of "V_{xy}" In Circuit Given Below Using Millman's Theorem. **[05]**



- [B]** Give an Account of Thevenin's Theorem. **[05]**

OR

- [C]** Discuss Maximum Power Transfer Theorem With Necessary Circuit Diagram. **[10]**

- Que 5 [A]** Discuss Parallel RL Circuit For AC Signals. Derive an Expression For the Total Impedance and Phase Angle of the Circuit. **[05]**

- [B]** Explain The Capacitor Response to Sinusoidal Signals. **[05]**

OR

- [C]** Discuss Series RL Circuit For AC Signals. Derive an Expression For the Total Impedance and Phase Angle of the Circuit. **[05]**

- [D]** The Current of 1.2 Amp Flows in a Coil With Inductance of 0.4 Henry, Determine the Energy Stored in Inductor. **[05]**

- Que 6 [A]** Draw and Explain the Circuit of the Parallel Resonance. Derive an Expression For the Resonance Frequency. **[05]**

- [B]** A Circuit Consist of Capacitor of 100pF Connected in Parallel With Coil of Resistance 5Ω and Inductance 100 μH. Calculate **[05]**

- 1) Resonance frequency
- 2) Q-factor
- 3) Bandwidth

OR

- [C]** Give an Account of Series Resonance Circuit. With Necessary Diagrams, Explain Inductor Response to AC Sinusoidal Signals. **[10]**

3

