

(100 &amp; A-20)

SEAT No. \_\_\_\_\_

કુલ પાનો: 3

(A.U.)

સરદાર પટેલ યુનિવર્સિટી

બી.એસ. સી, હિતીય સેમેસ્ટર

મંગળવાર, ૩ એપ્રિલ ૨૦૧૮

સમય: ૦૨:૦૦ થી ૦૪:૦૦ (સાંજ)

વિષય: (ભૌતિકશાસ્ક્રિપ્ટ) કોડ: US02CPHY02

શીર્ષક: ઇલેક્ટ્રોનિક્સ, ન્યુક્લિયર અને મોડર્ન ફિઝિક્સ

મહત્તમ માર્કેટ: 70

પ્રશ્ન. ૧ નીચે આપેલા બહુવિકલ્પી પ્રશ્નોના સાચા જવાબ લખો. [10]

૧ અર્ધ-તરંગ રેકટીફાયરમાં આર.એમ.એસ.પ્રવાહનું મૂલ્ય \_\_\_\_\_ હોય છે.

- a)  $\frac{I_m}{\sqrt{2}}$       b)  $\frac{I_m}{2}$   
 c)  $\sqrt{2} I_m$       d)  $2I_m$

૨ રેકટીફાયરના આઉટપુટના પલ્સેસન દૂર ફરવા \_\_\_\_\_ વપરાય છે.

- a) ટ્રાન્સફોર્મર      b) રેગ્યુલેટર  
 c) ફિલ્ટર      d) ટ્રાન્ઝિસ્ટર

૩ ટ્રાન્ઝિસ્ટરમાં સૌથી મોટો વિસ્તાર \_\_\_\_\_ નો હોય છે.

- a) બેઝ      b) એમીટર  
 c) સેન્ટર      d) ક્લેક્ટર

૪ પાવર ડાયોડ સામાન્ય રીતે \_\_\_\_\_ માંથી બનાવાય છે.

- a) તાંબુ      b) કાર્બન  
 c) જર્મનીયમ      d) સીલીકોન

૫ જો CE ટ્રાન્ઝિસ્ટરમાં ઈનપુટ જંક્શન ફોરવર્ડ બાયસમાં અને આઉટપુટ જંક્શન રીવર્સબાયસમાં હોય તો, તેનું Q-પોઇન્ટ આઉટપુટ લાલ્ભાણિક વકમાં \_\_\_\_\_ વિસ્તારમાં રહે છે.

- a) એક્ટિવ      b) સંતૃપ્તા (saturation)  
 c) કટ ઓફ      d) બ્રેક ડાઉન

૬ ૧ એટોમિક (અાણ્વિક) માસ યુનિટની સમકક્ષ ઉજ્જીવી કિમત \_\_\_\_\_ Mev હોય છે.

- a) 913.49      b) 931.49  
 c) 931.94      d) 921.49

૭ રેડીઓ કાર્બનનો અર્ધ-આયુષ્ય સમય \_\_\_\_\_ વર્ષ હોય છે.

- a) 5760      b) 5870  
 c) 5670      d) 5680

(1)

(C.P.T.Q)

- 8  $^{26}\text{Fe}^{56}$  માં ન્યુક્લોનની સંખ્યા \_\_\_\_\_ છે.

  - 26
  - 30
  - 56
  - 82

9 કોમ્પ્યુટરન અસરમાં પ્રકેરિત (scattered) ફોટોનની આવૃત્તિ \_\_\_\_\_ છે.

  - ધૃતે
  - વધે
  - અનંત બને
  - અચળ રહે

10  $e = 3$  માટે  $m_e$  ની કિમતો \_\_\_\_\_ હોય શકે.

  - 6
  - 8
  - 3
  - 7

પ્રશ્ન. ૨ નીચેના કોઈ પણ દસ પ્રશ્નોના ટુંકમાં જવાબ આપો.

[20]

- ૧ પાવર સપ્લાયનો બ્લોક ડાયાગ્રામ દોરી ઢેકમાં સમજુતી આપો.
  - ૨ ફિલ્ટર સર્કીટ એટલે શું? તેની જરૂરિયાત સમજાવો.
  - ૩ સેન્ટર-ટેપ પૂર્ણ તરંગ રેકટીફાયરની પરિપથ દોરો.
  - ૪ સિઝલ ડાયોડ એટલે શું? તેને ઢેકમાં સમજાવો.
  - ૫ ટ્રાન્ઝિસ્ટર માટે એમીટર છન્ઝેક્ષન ગુણોત્તર ( $\gamma$ ) અને બેઝ ટ્રાન્સપોર્ટેશન ફેક્ટર ( $\beta$ ) વ્યાખ્યાંયિત કરો.
  - ૬ npn અને pnp ટ્રાન્ઝિસ્ટર માટેના પરિપથ સંજ્ઞા દોરો.
  - ૭ ન્યુક્લીયસની ત્રિજ્યા મેળવવા માટેનું સુત્ર તારવો.
  - ૮ જરૂરી ઉદાહરણ આપી  $\alpha$  કણ ના ક્ષય થવાની પ્રક્રિયા સમજાવો.
  - ૯ ન્યુક્લીયસના અર્ધ-આયુ સમય માટે નીચે પ્રમાણેનું સુત્ર મેળવો.

$$\tau_{1/2} = 0.693/\lambda.$$

- 10 કોમ્પટન અસર દર્શાવતી ચિન્હો સાથેની આકૃતિ હોરો.

11. બોહર એટમ મોડેલ ની કોઈ પણ બે પૂર્વધારણાઓ લખો.

12. ક્ષ-કિરણ ફોટોન જયારે ઇલેક્ટ્રોન દ્વારા  $90^\circ$  ના ખૂણે પ્રકેરિત થાય ત્યારે તેની તરંગલંબાઈમાં આવતો તકાવત ગણો.

$$h = 6.62 \times 10^{-34} \text{ J-s}, m_0 = 9 \times 10^{-31} \text{ kg}, \text{ and } c = 3 \times 10^8 \text{ m/s}$$

પ્રશ્ન. 3 [A] અર્ધ-તરંગ રેકટિફિયર એટલે શું? અર્ધ-તરંગ રેકટિફિયર નો પરિપથ દોરો અને તેની રચના અને કાર્યપદ્ધતિ સમજાવો. [06]

[B] નીચેના પદો વ્યાખ્યાવિત કરો: (i) સીપલ ફેક્ટર (ii) રેક્ટીફિયરની કાર્યક્ષમતા. ઉપરાંત [04]  
સાબિત કરો કે પૂર્ણતરંગ રેક્ટીફિયરનો સીપલ ફેક્ટર 0.482 હોય છે.

અશ્વા

પ્રશ્ન. 3 [A] p-n ડાયોડ ની  $I \rightarrow V$  લાક્ષેણિકતાઓ ની આકાંક્ષા સહ વિભિન્નત ગાર્ગી દે

[06]

[B] प-डिल्टर विशेष टेक नोंद लामे

[04]

- પ્રશ્ન. ૪ [A] વેરેક્ટર ડાયોડ (Varactor diode) વિશે વિસ્તૃત નોંધ લખો. [05]  
[B] pnp ટ્રાન્ઝિસ્ટર માટેના  $\alpha_{dc}$  અને  $\beta_{dc}$  વ્યાપ્તાધિત કરો અને તે બંને વચ્ચેનો સંબંધ મેળવો. [05]

અધ્યવા

- પ્રશ્ન. ૪ [A] ઐનર ડાયોડ વોલ્ટેજ રેગુલેટર નો સંશ્લા સાથેનો પરિપથ દોરો અને તેની કાર્યપદ્ધતિ [05] સમજાવો.  
[B] LED વિશે વિસ્તૃત નોંધ લખો. [05]

- પ્રશ્ન. ૫ ન્યુક્લીયસ માટે ૧) બંધન ઉજ્જી ૨) એકમ ન્યુક્લિઓન દીઠ બંધન ઉજ્જી સમજાવો. [10]  
એકમ ન્યુક્લિઓન દીઠ બંધન ઉજ્જી વિશુદ્ધ દળ કમાંકનો ગ્રાફ દોરી તેની મુખ્ય વિશેષતા સમજાવો.

અધ્યવા

- પ્રશ્ન. ૫ લિઝિડ ફ્રોપ મોડેલની મદદથી એકમ ન્યુક્લિઓન દીઠ બંધન ઉજ્જાનું સુત્ર તારવો. [10]

- પ્રશ્ન. ૬ [A] દ્રવ્ય- તરંગો માટે E- બ્રોગ્લી તરંગલંબાઈનું  $\lambda = h/p$  સમીકરણ તારવો. [06]  
[B] વેક્ટર એટમ મોડેલ માટે સ્પેસ કવોન્ટાઇઝેશનનો વિચાર સમજાવો. [04]

અધ્યવા

- પ્રશ્ન. ૬ [A] પ્લાન્કના વિકિરણના નિયમનું સૂત્ર તરંગલંબાઈના સંદર્ભમાં મેળવો. [06]  
[B] પ્લાન્કના વિકિરણના નિયમ પરથી વેઇન અને રેલે-જુન્સનો નિયમ તારવો. [04]

(3)



[100/AZ0]  
Eng

SEAT No. \_\_\_\_\_

No. of pages: 2

SARDAR PATEL UNIVERSITY

B.Sc. 2<sup>nd</sup> Semester

Tuesday, 3<sup>rd</sup> April 2018

Time: 02:00 to 04:00 pm

Subject Code: (PHYSICS) US02CPHY02

Subject Title: Electronics, Nuclear and Modern Physics

Max Marks: 70

Que. 1 Write correct answer for each of the following MCQs.

[10]

1 The rms value of current for the half-wave rectifier is \_\_\_\_\_.

- a)  $\frac{I_m}{\sqrt{2}}$       b)  $\frac{I_m}{2}$   
c)  $\sqrt{2} I_m$       d)  $2I_m$

2 \_\_\_\_\_ is used to remove the pulsation in the output of the rectifier.

- a) Transformer      b) Regulator  
c) Filter      d) Transistor

3 The largest region in the transistor is known as \_\_\_\_\_.

- a) base      b) emitter  
c) centre      d) collector

4 Power diodes are generally made from \_\_\_\_\_.

- a) copper      b) carbon  
c) germanium      d) silicon

5 For a CE transistor, if the input junction is forward biased and the output junction is reverse biased, its Q point will remain in the \_\_\_\_\_ region in the output characteristics.

- a) active      b) saturation  
c) cut-off      d) breakdown

6 The energy equivalent to one atomic mass unit is \_\_\_\_\_ Mev.

- a) 913.49      b) 931.49  
c) 931.94      d) 921.49

7 The half life time of a radio carbon is \_\_\_\_\_ years.

- a) 5760      b) 5870  
c) 5670      d) 5680

8 The number of neutrons in  $^{56}_{26}\text{Fe}$  is \_\_\_\_\_.

- a) 26      b) 30  
c) 56      d) 82

9 In Compton effect the frequency of scattered photon \_\_\_\_\_.

- a) decreases      b) increases  
c) becomes infinite      d) remains unchanged

10 For  $\ell = 3$ ,  $m_\ell$  can take \_\_\_\_\_ values.

- a) 6      b) 8  
c) 3      d) 7

**Que. 2 Write answers of any ten questions in brief.**

[20]

- 1 Draw the block diagram of a power supply with a brief note.
- 2 What is a filter circuit? Why it is required?
- 3 Draw the circuit diagram of the centre-tap FWR.
- 4 What are signal diodes? Explain it in brief.
- 5 Define Emitter injection ratio ( $\gamma$ ) and base transportation factor ( $\beta$ ) for the transistor.
- 6 Draw the circuit symbols for the npn and pnp transistor.
- 7 Obtain the formula for radius of the nucleus.
- 8 Explain  $\alpha$ -decay process giving necessary example.
- 9 Derive the formula for half life time  $\tau_{1/2} = 0.693/\lambda$ .
- 10 Draw a labelled diagram for Compton effect.
- 11 Mention any two postulates of Bohr atom model.
- 12 Calculate change in wavelength of X-ray photon scattered through an angle of  $90^\circ$  by a free electron.

Given:  $h = 6.62 \times 10^{-34}$  J-s,  $m_0 = 9 \times 10^{-31}$  kg, and  $c = 3 \times 10^8$  m/s

**Que. 3 [A] What is a half-wave rectifier? Draw the labelled diagram of the half-wave rectifier and explain its construction and working. [06]**

**[B] Define the terms: (i) Ripple factor, (ii) Rectification efficiency. Also show that [04] the value of the ripple factor for the full-wave rectifier is 0.482.**

**OR**

**Que. 3 [A] Discuss the  $I \rightarrow V$  characteristics of a p-n junction diode with proper [06] diagrams.**

**[B] Write a note on  $\pi$ -filter. [04]**

**Que. 4 [A] Write a detailed note on Varactor diode. [05]**

**[B] Define  $\alpha_{dc}$  and  $\beta_{dc}$  for a pnp transistor. Derive relation between them. [05]**

**OR**

**Que. 4 [A] Draw the labeled diagram of a Zener diode voltage regulator circuit. Also [05] explain its working.**

**[B] Write a detailed note on LED. [05]**

**Que. 5 For atomic nuclei explain (1) Binding energy (2) Binding energy per nucleon. [10] Draw the graph of binding energy per nucleon versus mass number and discuss its salient features.**

**OR**

**Que. 5 Obtain the formula for binding energy per nucleon with the help of liquid [10] drop model.**

**Que. 6 [A] Derive the formula for De-Broglie wavelength of matter waves  $\lambda = h/p$ . [06]**

**[B] Explain the concept of space quantization for vector atom model. [04]**

**OR**

**Que. 6 [A] Derive the formula for Planck law of radiation in terms of wavelength. [06]**

**[B] Derive Wien's law and Rayleigh-Jeans law from Planck's law of radiation. [04]**