

SARDAR PATEL UNIVERSITYB.Sc. (6th Sem) Examination - March/April-2016 CBCS**Programmable Logic Controller (PLC) - 2US06CINS04 (Instrumentation)**Monday, 4th April, 2016

2:30 pm - 5:30 pm

Maximum Marks: 70

Que 1 Each question below gives a multiple choice of answers. Choose the most appropriate one. 10

- 1 The ____ will supply the trigger pulse for the D, T, and J-K Flip Flops.
 - A. One shot
 - B. Sequencer
 - C. Timer
 - D. None of these
- 2 Timers usually fall into ____ category/ies depending on the PLC manufacturer.
 - A. Retentive
 - B. Non - retentive
 - C. Both a) and b)
 - D. None of these
- 3 PLC ____ is fundamentally counter with some extra features and some minor differences.
 - A. Timed One Shot
 - B. Sequencer
 - C. Both a) and b)
 - D. None of these
- 4 LD commands are terminated with either ____ command or a coil command.
 - A. LD
 - B. STO
 - C. Both a) and b)
 - D. None of these
- 5 The STO command tells the controller that the previous logic is to control the coil that follows the ____ command.
 - A. LD
 - B. STO
 - C. ENTER
 - D. None of these
- 6 The termination command for a line of code is generally _____.
 - A. LD
 - B. ENTER
 - C. STO
 - D. None of these
- 7 An opto-isolator is device consisting of _____.
 - A. Light producing element
 - B. Light sensing element
 - C. Both a) and b)
 - D. None of these
- 8 There are several types of solid state outputs available with PLCs, such as _____.
 - A. Transistor
 - B. Triac
 - C. Both a) and b)
 - D. None of these
- 9 The ____ of an A/D operation determines the number of digital values the converter is capable of discerning over its range.
 - A. Input range
 - B. Number of bits of Resolution
 - C. Both a) and b)
 - D. None of these
- 10 If the voltage being measured will never be negative, then ____ input is the best choice.
 - A. Unipolar
 - B. Bipolar
 - C. Both a) and b)
 - D. None of these

PTO

Que 2 Short Questions (Attempt any TEN)**20**

- 1 Explain the use of R-S Flip Flop in PLC with suitable LADDER Rung.
- 2 Draw the LADDER diagram for D Flip Flop.
- 3 What is Flasher?
- 4 What is PLC Mnemonic Programming Code?
- 5 Explain briefly Entering of Normally Closed Contacts in PLC LADDER Rung.
- 6 Explain: LD Command.
- 7 Draw typical PLC Transistor Output Wiring diagram.
- 8 Draw typical PLC Non - Isolated Input Wiring diagram.
- 9 Explain briefly on PLC Power Connection.
- 10 What do you mean by PLC 'Input Range'?
- 11 Explain briefly what 'Number of Bits of Resolution' is.
- 12 Describe Analog Data Handling with respect to PLC.

- Que 3** **A** Explain Timed One Shot. **05**
 B Write a note on Retentive Timer. **05**
- OR**
- C** Give an account of Sequencers. **05**
 D Write a note on Counters. **05**

- Que 4** **A** Explain PLC Complex Ladder Rung. **05**
 B Write a note on OR Ladder Rung. **05**
- OR**
- C** Write a note on PLC Simple Branches. **05**
 D Write a note on AND Ladder Rung. **05**

- Que 5** **A** Write a detailed note on PLC Isolated Inputs. **10**
- OR**
- B** Give an account of PLC Solid State Outputs. **10**

- Que 6** **A** Write a note on 'Analog (D/A) Output' with respect to PLC. **05**
 B A 10 - bit bipolar analog input has an input range of -5 to +5 volts. If the converter outputs the binary number 0110111101_2 , what is the voltage being read? **05**
- OR**
- C** Explain Analog Input Potential Problems associated with PLCs. **05**
 D A voltage of 3.500 volts is applied to an 8 - bit, 5 volt unipolar analog input of a PLC. Using monitor software, the PLC analog input register shows a value of 263_8 . Is the analog input working correctly? **05**

Best Wishes