

SARDAR PATEL UNIVERSITY
BSc (VI Sem.) Examination
Tuesday, 9th April 2013
3 - 6 pm
US06CELE02 – Digital System II

Total Marks: 70

Note: Figures to the right indicate full marks.

- Q.1 Multiple choice questions. [10]
- (1) A storage element is called _____.
 (a) Cell (b) Device (c) Disk
 - (2) The operational amplifier is used to produce weighted sum of the _____.
 (a) Analog input (b) Digital input (c) BCD input
 - (3) Retrieving data from the memory is called _____.
 (a) Reading memory (b) Writing memory (c) Modifying memory
 - (4) In DAC converter analog output= _____.
 (a) $K \times$ digital output (b) Digital \times Analog output
 (c) $K \times$ digital input
 - (5) The ECL RAM has open _____ outputs.
 (a) Base (b) Emitter (c) Collector
 - (6) A certain 4 bit DAC uses binary weighted resistors. If the MSB resistor is $100 \text{ k}\Omega$ the LSB resistor will be _____.
 (a) $25 \text{ k}\Omega$ (b) $800 \text{ k}\Omega$ (c) $12.5 \text{ k}\Omega$
 - (7) The another name of peripheral memory is _____.
 (a) Main memory (b) Magnetic memory (c) Auxiliary memory
 - (8) Resolution= _____.
 (a) Step Size (b) Full Scale Output (c) 2^N
 - (9) The Dynamic RAM are fabricated using only _____.
 (a) MOS (b) BJT (c) NMOS
 - (10) In voltage to Frequency type ADC, the output Frequency is proportional to _____.
 (a) Digital input (b) Analog input (c) both (a) and (b)

- Q.2 Answer **Any Ten** in brief. [20]
- (1) Define main and peripheral memory.
 - (2) Give the classification of ROM.
 - (3) Give the difference between program and data memory.
 - (4) List the types of ROM.
 - (5) What are the applications of SRAM?
 - (6) State the differences between Static RAM and Dynamic RAM.
 - (7) Draw the block diagram of 3 bit flash type ADC converter.
 - (8) List the Parameters of DAC.
 - (9) A 7 bit DAC has a step size of 50mv. Determine the full scale output voltage and percentage resolution.
 - (10) Draw the block diagram of modified Flash type A/D converter.

- (11) An ADC has a total conversion time of 200μ sec. What is the highest Frequency that its analog input should be allowed to contain?
- (12) Draw the pin configuration of the ADC 0801.
- Q.3
- (a) Explain RAMs, ROMs and PROMs. [05]
- (b) Explain ROM timing diagram in detail [05]
- OR**
- Q.3
- (a) Explain the role of memory in a Computer System. [05]
- (b) Explain ROM Organisations. [05]
- Q.4
- (a) Explain Tristate Switch in detail. [05]
- (b) List all the Static RAMs and explain one of them. [05]
- OR**
- Q.4 Explain types of ROMs in detail. [10]
- Q.5
- (a) Explain R-2R ladder type DAC in detail. [06]
- (b) Explain tracking type ADC converter. [04]
- OR**
- Q.5
- (a) Explain Counter type ADC converter. [06]
- (b) Explain the Parameters of DAC in detail. [04]
- Q.6 Explain Voltage to time A/D converter. [10]
- OR**
- Q.6 Explain Voltage to Frequency type A/D converter. [10]

* * *