

[62]

SARDARPATEL UNIVERSITY V.V.NAGAR

T.Y.B.Sc. Sem-VI EXAMINATION

SUB. CODE:-US06CELE02

Digital Systems IIIDATE:-27/03/2019, ^{Wednesday} TIME:-10:00 am to 01:00 pm

MARKS-70

- Q-1 Choose correct answer [10]**
- V/F type A/D converter _____ is changing.
(A) Time (C) Frequency.
(B) Phase (D) None of these
 - V/T type A/D converter _____ is constant.
(A) Time (C) Frequency.
(B) Phase (D) None of these
 - Flash/Comparator type A/D converter is _____ converter.
(A) Fastest (C) Medium
(B) Slowest (D) None of these
 - D/A converter is part of _____ converter,
(A) A/D (C) D/A
(B) A/F (D) None of these
 - Tristate switch has Low, High and _____ state.
(A) Floating (C) short circuit
(B) open (D) None of these
 - In Bipolar ROM before programming all data are _____.
(A) 1 (C) 0
(B) blanks (D) None of these
 - In static Bipolar RAM 0 & 1 are sensed by presence of _____.
(A) Current (C) Voltage
(B) Resistor (D) None of these
 - The control input CS stands for _____.
(A) Chip select (C) chip stop
(B) chip chops (D) None of these
 - BJT memory is _____ than MOS memory,
(A) Faster (C) Slower
(B) Not working (D) None of these
 - An IC ADC 0801 has _____ bit output.
(A) Three (C) Eight
(B) Four (D) None of these

Q-2 Short answer type question. (any ten) [20]

- Explain what do you understand by program memory.
- Explain what do you understand by data memory.
- Give classification of Read and Write memories drawing diagram.
- Draw a figure of single transistor dynamic memory cell.
- Explain Address Multiplexing.
- Draw the diagram of static bipolar (TTL) RAM cell.
- Draw the circuit of weighted resistor type DAC.
- Draw the o/p waveforms of counter type ADC.
- List the parameters of DAC & Explain any one in brief.
- Draw the circuit of 3 bit flash type A/D converter.
- List A/D converter specifications, and explain any one in brief.
- List different types of A/D converter.

- Q.3 Write a note on RAM,ROM & PROM. [10]
OR
Q.3 Give an account ROM organization also draw ROM block diagram and explain it. [10]
- Q.4 Give an account of Programmable read only memory. [10]
OR
Q.4 Give an account of Tristate-Switch. [10]
- Q.5 Draw the circuit of R-2R ladder type DAC, explain its working in detail. [10]
OR
Q.5 Give an account of counter type A/D converter. [10]
- Q.6 Give an account of V/F type A/D converter. [10]
OR
Q.6 Give an account of V/T type A/D converter. [10]

————— X —————