

Que 2 Short Questions (Attempt Any Ten)

[20]

- 1 What is flasher?
- 2 Write on cascading timers.
- 3 Explain timed one shot.
- 4 Explain entering of normally closed contacts with necessary ladder diagram.
- 5 Draw the ladder diagram for a program that will accept inputs from switches IN1, IN2, IN3, IN4 and IN5 and will energize coil OUT123 when one and only one of the inputs in ON.
- 6 Draw the ladder diagram for exclusive-OR logic function.
- 7 Briefly explain output wiring.
- 8 Write briefly on solid state outputs.
- 9 Write on isolated inputs.
- 10 A temperature sensor outputs 0-10 volts dc for a temperature span of 0-100 °C. What is the bit resolution of a PLC analog input that will digitize a temperature variation of 0.1 °C?
- 11 A 10-bit bipolar analog input has an input range -5 to +5 volts. If the converter outputs the binary number 0110111101₂, what is the voltage being read?
- 12 Explain analog data handling.

Que 3 [A] Explain timed sequencer. [05]

[B] With necessary ladder diagram, explain RS flip flop. [05]

OR

[A] Write a detailed note on timers with necessary ladder diagrams. [10]

Que 4 [A] Draw ladder diagram of AND function. Write mnemonic codes for AND function. [05]

[B] Write a note on complex branches with necessary ladder diagram. [05]

OR

[A] Draw ladder diagram of OR function. Write mnemonic codes for OR function. [05]

[B] Write a note on simple branches with necessary ladder diagram. [05]

Que 5 [A] Write a detailed note on PLC input wiring with necessary diagrams. [10]

OR

[A] Give an account of PLC relay outputs with necessary diagrams. [10]

Que 6 [A] Discuss constant offset error and percentage offset error. [05]

[B] Write a note on analog (D/A) output. [05]

A 12-bit, 10 volt bipolar analog output has a maximum output current capability of 20 mA. It is connected to a load that has a resistance of 330 ohms. Will this system work correctly?

OR

[A] Enlist analog input potential problems. Explain unstable reading in detail. [05]

[B] Give an account of input range and number of bits of resolution with respect to analog (A/D) input. [05]