

[72]  
[E86J]

## SARDAR PATEL UNIVERSITY

B.Sc. Examination, SEM - III : January - 2021

## COMPUTER SCIENCE

## US03ECSC01: DIGITAL COMPUTERS ELECTRONICS

Thursday, 7<sup>th</sup> January - 2021

Time : 2:00pm to 4:00pm

Max. Marks: 70

[10]

## Q.1 Multiple choice of Question

1.  $A+A'B+A'B'=?$   
A. 1    B. 0    C. A    D.  $A'$
2. An invert gate is also called a \_\_\_\_\_ gate.  
A. NOR    B. NAND    C. NOT    D. XNOR
3. The OR gate has two or more input signals. If any input is \_\_\_\_\_, the output is high.  
A. high    B. low    C. high and low    D. none
4. The relationship between a function and its binary variables can be represented in \_\_\_\_\_.  
A. truth table    B. decoder    C. encoder    D. multiplexer
5. \_\_\_\_\_ is way to simplify the equation.  
A. Boolean Algebra    B. K-MAP    C. Both    D. None
6. In k-map, pair eliminates \_\_\_\_\_ variable.  
A. two    B. three    C. one    D. four
7. In half adder the output of XOR gate is \_\_\_\_\_.  
A. carry    B. reminder    C. sum    D. None
8. A \_\_\_\_\_ is logic circuit that can add two binary numbers.  
A. binary adder    B. decoder    C. AND gate    D. OR gate
9. In D flip-flop, when CLK is low then input is \_\_\_\_\_.  
A. High    B. Don't care    C. Low    D. Not Change
10. A register is a group of \_\_\_\_\_ that work together as a unit.  
A. flip-flop    B. decoder    C. multiplexer    D. gates

## Q.2 Fill in the blank and True/False.

[08]

1. The \_\_\_\_\_ gate has two or more input signals. All inputs must be high to get a high output.
2. The EX-NOR gate has two or more input signals. All inputs must be same to get a high output. [True / False]
3. In Comparator, \_\_\_\_\_ gate is use for comparing bits in word.
4. An encoder is a combinational circuit that converts binary information from the  $2^n$  coded inputs to  $n$  outputs. [True / False]
5. Half adder is logic Circuit that adds \_\_\_\_\_ Digit at a time.
6. A gate is a logic circuit with one or more input signals but only one output signal. [True / False]
7. In shift left register, the arrival of the first rising clock edge sets the \_\_\_\_\_ flip-flop.
8. In D flip-flop, when CLK is high then output is high. [True / False]

[13]

[P.T.O.]

**Q.3 Answer the following questions in SHORT. (Any 10)**

[20]

1. Explain Associative law.
2. Explain distributive law.
3. Draw the circuit for  $(A \cdot B)'$ .
4. Explain Quads in k-map with example.
5. Explain Pair in k-map with example.
6. Explain Octet in k-map with example.
7. What is multiplexer?
8. Explain full adder.
9. Draw logic circuit of  $4 \times 1$  multiplexer.
10. Draw graphical symbol of D flip-flop.
11. Explain shift right register.
12. Draw logic diagram of D flip-flop.

**Q.4 Answer the following questions in LONG. (Any 4)**

[32]

1. Explain DeMorgan's first and second theorem.
2. Explain NAND, bubbled OR and EX-OR gates.
3. Simplify  $F(A,B,C,D) = \prod(1,2,5,6,8,12,14)$  using k-map.
4. Define decoder. Explain  $3 \times 8$  decoder in detail.
5. Explain  $8 \times 1$  multiplexer in detail.
6. Explain binary adder-subtractor.
7. Explain controlled buffer register in detail.
8. Explain ring counters in detail.

[2]

SEAT No. \_\_\_\_\_

[72]

સરદાર પટેલ યુનિવર્સિટી

બી.એસ.સી. પરીક્ષા, SEM - III: જાન્યુઆરી 2021

કમ્પ્યુટર સાયન્સ

US03ECSC01: ડિજિટલ કમ્પ્યુટર્સ ઇલેક્ટ્રોનિક્સ

તૃતીય વાર, જાન્યુઆરી 2021

સમય: 2:00 થી બપોરે 4:00 સુધી

મેક્સ. ગુણ: 70

પ્રશ્નના. 1 પ્રશ્નની બહુવિધ પસંદગી

[10]

1.  $A + A'B + A'B' = ?$

એ. 1 બી. 0 સી. એ ડી. એ'

2. એક inલટું ગેટ \_\_\_\_\_ દ્વારા પણ કહેવામાં આવે છે.

એ. નોર બી. નંદ સી. ડી. એક્સનોર

3. ઓફાર ગેટમાં બે કે તેથી વધુ ઇનપુટ સિગનલ હોય છે. જો કોઈ ઇનપુટ \_\_\_\_\_ છે, તો  
આઉટપુટ વધારે છે.

એ. ઉચ્ચ બી. લો સી. ઉચ્ચ અને નીચું ડી. કંઈ નહીં

4. કોઈ ફંક્શન અને તેના ડિસંગી ચલો વચ્ચેનો સંબંધ હોઈ શકે છે

માં 2જી

એ. સત્ય કોષ્ટક બી. ડિકોડર સી. એન્કોડર ડી. મલ્ટિપ્લેક્સર

5. સમીકરણને સરળ બનાવવાની આ \_\_\_\_\_ રીત.

એ. બુલિયન બીજગાળિત બી. કે-એમએપી સી. બંને ડી. કંઈ નહીં

6. કે-નક્શામાં, જોડી \_\_\_\_\_ ચલને દૂર કરે છે.

એ. બે બી. ત્રણ સી. એક ડી. ઝોર

7. અડધા એડિટરમાં XOR ગેટનું આઉટપુટ \_\_\_\_\_ છે.

એ. વહન બી. રીમાઇન્ડર સી. સરવાળો ડી. કંઈ નહીં

8. એક \_\_\_\_\_ is લોજિક સર્કિટ જે બે બાઈનરી નંબરો ઉમેરી શકે છે.

એ. ડિસંગી એડિ. બી ડિકોડર સી. AND ગેટ ડી. OR ગેટ

9. ડી ફિલ્પ-ફિલોપમાં, જ્યારે સીએલકે નીચી હોય ત્યારે ઇનપુટ \_\_\_\_\_ હોય છે.

એ. ઉચ્ચ બી. કાળજી લેશો નહીં. સી. નીચી ડી. બદલાતી નથી

10. રજિસ્ટર એ \_\_\_\_\_ નો જીથ છે જે એકમ તરીકે એક સાથે કાર્ય કરે છે.

એ. ફિલ્પ-ફિલોપ બી ડિકોડર સી. મલ્ટિપ્લેક્સર ડી. ગેટ્સ

પ્રશ્ન.2 ખાલી અને સાચું/ખોટું ભરો:

[08]

1. \_\_\_\_\_ દરવાજામાં બે કે તેથી વધુ ઇનપુટ સંકેતો છે. બધા ઇનપુટ્સ આવશ્યક છે  
ઉચ્ચ આઉટપુટ મેળવવા માટે ઉચ્ચ હોવું જોઈએ.

2. એક્સ-નોર ગેટ પાસે બે અથવા વધુ ઇનપુટ સિજનલ છે. બધા ઇનપુટ્સ આવશ્યક છે  
ઉચ્ચ આઉટપુટ મેળવવા માટે સમાન બનો. [સાચું/ખોટું]

3. સરખામણી કરનારમાં, \_\_\_\_\_ દરવાજા એ શબ્દમાં બીટસની તુલના કરવા માટે વપરાય છે.

4. એન્કોડર એ સંયુક્ત સર્કિટ છે જે 2 એન કોડે ઇનપુટ્સમાંથી બાઈનરી માહિતીને એન

83

[P.T.O.]

આઉટપુટમાં ઉપાંતરિત કરે છે. [સાચું/ ખોટું]

5. અડધો એડ્રેસર એ લોજિક સર્કિટ છે જે એક સમયે \_\_\_\_\_ અંકનો ઉમેરો કરે છે.
6. દરવાજો એ એક અથવા વધુ ઇનપુટ સિન્ઝલ સાથેનો લોજિક સર્કિટ છે પરંતુ માત્ર એક જ આઉટપુટ સિન્ઝલ [સાચું/ ખોટું]
7. પાણી ડાબી રજિસ્ટરમાં, પ્રથમ વધતી ઘડિયાળની ધારનું આગમન સુયોજિત કરે છે \_\_\_\_\_ ફ્લીપ ફ્લોપ.

8. ડી ફ્લીપ-ફ્લોપમાં, જ્યારે સીએલકે વધારે હોય ત્યારે આઉટપુટ વધારે હોય છે. [સાચું/ ખોટું]

પ્રશ્ન.3 ટ્રેકમાં નીચેના પ્રશ્નોના જવાબો આપો. (કોઈપણ 10)

[20]

1. સહયોગી નીચા સમજાવો.
2. વિતરિત નીચા સમજાવો.
3. (A B) 'માટે સર્કિટ દોરો.
4. ઉદાહરણ સાથે કે-મેપમાં ક્વાડ્સ સમજાવો.
5. ઉદાહરણ સાથે કે-ન્કશામાં જોડીને સમજાવો.
6. ઉદાહરણ સાથે કે-મેપમાં ક્રેટને સમજાવો.
7. મલ્ટિપ્લેક્સર એટલે શું?
8. સંપૂર્ણ એડ્રેયર સમજાવો.
9.  $4 \times 1$  મલ્ટિપ્લેક્સરનું લોજિક સર્કિટ દોરો.
10. ડી ફ્લીપ-ફ્લોપનું ગ્રાફિકલ પ્રતીક દોરો.
11. પાણી જમણી રજિસ્ટર સમજાવો.
12. ડી ફ્લીપ-ફ્લોપનું લોજિક આકૃતિ દોરો.

પ્રશ્ન.4 લાંબામાં નીચેના પ્રશ્નોના જવાબો આપો. (કોઈપણ 4)

[32]

1. ડિમોર્ગનના પ્રથમ અને બીજા પ્રમેયને સમજાવો.
2. નંદ, પરપોટાવાળા OR અને EX-OR દરવાજા સમજાવો.
3. કે-મેપનો ઉપયોગ કરીને એક (એ, બી, સી, ડી) = Simp (1,2,5,6,8,12,14) સરળ બનાવો.
4. ડીકોડર વ્યાખ્યાયિત કરો.  $3 \times 8$  ડીકોડરને વિગતવાર સમજાવો.
5.  $8 \times 1$  મલ્ટિપ્લેક્સરને વિગતવાર સમજાવો.
6. દ્વિસંગી એડિટર-સબટ્રેક્ટર સમજાવો.
7. નિયંત્રિત બફર રજિસ્ટરની વિગતવાર સમજાવો.
8. રિંગ કાઉન્ટરને વિગતવાર સમજાવો.

[4]