

[85]

Seat No : _____

No. of Printed Pages : 02

SARDAR PATEL UNIVERSITY
S.Y.B. Sc. Examination, Semester III
Date & day: 26-11-2019 & Tuesday
Time: 02:00 to 05:00 pm
Physics Course Code- US03CAPH22

Course Title-Digital Electronics & Optoelectronic Devices

Total Marks:70

Q-1 Write answers to the following multiple choice questions in your answer book by selecting the proper option. [10]

- (1) A group of 8 bit is known as-
(a) A nibble (b) a byte (c) a bit (d) an octal number
- (2) In X-NOR gate, both the inputs are high then the output is-
(a)High (b) Low (c) undefined (d) both a and b
- (3) The number of adjacent cells each cell in an n variables, a K- map can have is-
(a) n-1 (b) n (c) n+1 (d) 2n
- (4) $(734)_8 = (?)_{16}$
(a) C 1 D (b) D C 1 (c) 1 C D (d) 1 D C
- (5) The device used to store the one bit data is known as-
(a) Flip Flop (b) Register (c) decoder (d) Encoder
- (6) How many flip-flops are required to produce a divide-by-128 device?
(a) 1 (b) 4 (c) 6 (d) 7
- (7) Which of the following logic circuits accepts two binary digits on inputs, and produces two binary digits, a sum bit and a carry bit on its outputs?
(a) Full-adder (b) half- adder (c) Serial adder (d) parallel adder
- (8) The number of control lines for 16 to 1 multiplexer is
(a) 2 (b) 4 (c) 3 (d) 5
- (9) The combined package of LED and a photodiode is known as-
(a) Opto-couplers (b) Opto-isolator (c) Optically coupled isolator (d) All of these
- (10) A photodiode is used in reverse bias because-
(a) Majority of electron-hole pairs swept are reversed across the junction
(b) Only one side is illuminated
(c) Reverse current is small compared to photocurrent
(d) Reverse current is large compared to photocurrent

Q-2 Answer the following questions in brief. (Answer any Ten Questions)

[20]

- (1) Convert the $(1001011)_2$ to octal.
- (2) Add the binary numbers 1101.101 and 111.011
- (3) Draw the truth table of X-NOR gate.
- (4) Write the Commutative and distributive laws of Boolean algebra.
- (5) Show that - $AC + \bar{A}B = (A + B)(\bar{A} + C)$
- (6) Sketch the three variable K-map and there expression.
- (7) Sketch the full adder circuit diagram.
- (8) Write few application of multiplexer.
- (9) Why we need a parity bit checker?
- (10) Compare the photo cell and Solar cell.
- (11) What is an optocoupler?
- (12) Sketch the LED seven segment display.

(P.T.O.)

- Q-3 (a) Prove the De Morgan's theorem using truth table method. [6]
 (b) Compare the exclusive OR and Exclusive NOR gate. [4]
- OR**
- Q-3 (a) Add the following numbers. [6]
 (i) $(173)_{16} + (265)_{16}$ (ii) $(777)_8 + (677)_8$ (iii) $(111011)_2 + (101101)_2$ [4]
 (b) Convert $(B36.ABC)_{16}$ to decimal number.
- Q-4 (a) Reduce the expression- [6]
 (i) $AB + A(B + C) + \bar{B}(B + D)$ (ii) $(X+Y+Z)(\bar{X} + \bar{Y} + \bar{Z})$ [4]
 (b) Explain the J-K flip flop in detail.
- OR**
- Q-4 (a) Prove that [6]
 (i) $\overline{ACB} + \overline{(A + B + C)} = \bar{A}\bar{B}\bar{C}$ (ii) $\overline{ABC + \bar{A}\bar{B} + BC} = \bar{A}\bar{B}$ [4]
 (b) Reduce the expression $f = \sum(2,3,6,7,8,10,11,13,14)$ using K- map.
- Q-5 (a) What is parity bit checker? Draw the figure for even and odd parity checker. [6]
 (b) Discuss the 4 bit adder and subtractor. [4]
- OR**
- Q-5 (a) Explain the Encoder with an example of Octal to BCD encoder in detail. [6]
 (b) Distinguish in between full adder and full-subtractor. [4]
- Q-6 (a) Write a detail note on Light Emitting Diode's operation and construction and its [6]
 application. [4]
 (b) Sketch the typical construction and illumination characteristics for a [4]
 photoconductive cell. Explain its operation.
- OR**
- Q-6 (a) Give a brief note on the Working, operation and characteristics of Laser diode. [6]
 (b) Sketch characteristics for a phototransistor, and explain how the device [4]
 operates.



②