

91/A-24  
Eng

Seat No : \_\_\_\_\_

No. of Printed Pages : 02

SARDAR PATEL UNIVERSITY

3<sup>rd</sup> Semester B. Sc. (Under CBCS) Examination-2019

Tuesday, 26<sup>th</sup> Nov-2019

Time: From 2:00pm to 5:00 pm

Subject: PHYSICS [US03CPHY02]

[Basic Solid State Electronics] Total Marks: 70

N.B: (i) All the symbols have their usual meanings.

(ii) Figures at the right side of questions indicate full marks.

Q-1 Answer the following Multiple Choice Questions.

[10]

- (1) The transistor parameters are \_\_\_\_\_.  
(a) temperature dependent (b) pressure dependent  
(c) P-N junction dependent (d) None of above
- (2) In the voltage divider biasing network, the Q-point of the transistor can be made almost independent of \_\_\_\_\_.  
(a)  $\beta$  (b)  $\alpha$  (c) current (d) voltage
- (3) Transistors are used in \_\_\_\_\_.  
(a) Zener diode (b) Amplifier (c) P-N junction diode (d) None of above
- (4) Which of the following h-parameter gives forward current ratio of a C-E transistor?  
(a)  $h_{re}$  (b)  $h_{fe}$  (c)  $h_{ie}$  (d)  $h_{oe}$
- (5) If  $v_i$  and  $v_o$  are respective input and output voltages of an amplifier then the voltage gain  $A_v$  is \_\_\_\_\_.  
(a)  $v_i + v_o$  (b)  $v_i - v_o$  (c)  $\frac{v_o}{v_i}$  (d)  $\frac{v_i}{v_o}$
- (6) An amplifier circuit of a current gain 100 has 5mA input. The value of output current is \_\_\_\_\_.  
(a) 50 mA (b) 500 mA (c) 5000 mA (d) 5 mA
- (7) Which of the following is the demerit of negative feedback amplifier?  
(a) Reduction in band with (b) Reduction in noise  
(c) Reduction in gain (d) Reduction in distortion
- (8) The voltage gain of emitter follower is always \_\_\_\_\_.  
(a) greater than unity (b) greater than two  
(c) less than unity (d) infinite
- (9) Barkhausen criterion for oscillator is \_\_\_\_\_.  
(a)  $A\beta = 1$  (b)  $A\beta < 1$  (c)  $A\beta > 1$  (d) None of these
- (10) The input impedance of a negative feedback amplifier is increased by factor \_\_\_\_\_.  
(a)  $[A\beta + 1]$  (b)  $1/A\beta$  (c)  $[A\beta - 1]$  (d) None of above

(1)

(P.T.O)

- Q-2 Answer the following questions in short : (Attempt Any Ten) [20]**
- (1) What is thermal run away of transistor? Explain with proper diagram.
  - (2) State requirements of a good biasing circuit.
  - (3) Draw neat and clean labeled circuit diagram for simple biasing using PNP transistor.
  - (4) Give the phase relationship between input and output in C-E mode of NPN transistor.
  - (5) A multistage amplifier consists of three stages. The voltage gain of the stages are 30, 50, and 80. Calculate the overall voltage gain in dB.
  - (6) Define small signal amplifier and write its application.
  - (7) Write basic requirements of an oscillator circuit.
  - (8) Give classification of oscillator in terms of generation of waveform.
  - (9) Differentiate between an amplifier and an oscillator.
  - (10) Distinguish between positive and negative feedback.
  - (11) Draw the block diagram of : (1) Voltage-Shunt feedback (2) Current-Shunt feedback
  - (12) Why positive feedback is not used in amplifier circuit?
- Q-3 (a) What is Fixed bias circuit? Explain how operating point of a fixed bias circuit is determined. [06]**
- (b) A collector to base bias circuit having  $V_{CC} = 10\text{ V}$ ,  $R_B = 500\text{ K}\Omega$ ,  $R_C = 500\text{ }\Omega$  and  $\beta$  of the transistor equal to 100. Find its collector current and voltage. Determine position of the operating point. [04]**
- OR**
- Q-3 (a) What is voltage divider biasing circuit? Using approximate analysis, explain how to determine operating point of such circuit. [06]**
- (b) Discuss emitter bias circuit using NPN transistor with proper circuit diagram [04]**
- Q-4 (a) Explain the analysis of single stage transistor amplifier with ac equivalent circuit. Also obtain expression for (a) voltage gain (b) current gain (c) power gain. [06]**
- (b) Draw the neat and clean circuit diagram for single stage transistor amplifier. [04]**
- OR**
- Q-4 (a) What are h-parameters? Explain development of h- parameter equivalent circuit for CE configuration. [06]**
- (b) Define multistage amplifier. Explain its need and obtain an expression for voltage gain of multistage amplifier. [04]**
- Q-5 (a) State advantages of negative feedback in amplifier. Explain any one advantage of negative feedback in detail. [05]**
- (b) Discuss RC coupled amplifier without bypass capacitor using NPN transistor. [05]**
- OR**
- Q-5 (a) Discuss voltage gain of feedback amplifier using proper circuit diagram. [05]**
- (b) Write a note on "Emitter Follower". [05]**
- Q-6 Write notes on Hartley oscillator and Colpitt's oscillator. [10]**
- OR**
- Q-6 Write basic principles of RC oscillators. Discuss Phase-Shift Oscillator and Wein Bridge Oscillator with proper circuit diagram. [10]**

