

29

SEAT No. _____

No. of Printed Pages : 2

SARDAR PATEL UNIVERSITY

B.Sc. INSTRUMENTATION (V)

SEM-III, NOVEMBER-2018 EXAMINATION

SUB. CODE:-US03CINV02

SUB: Electronic Circuit & Optical Device-I

DATE:-30/11/2018, Friday

TIME:-2:00 pm to 5:00 pm

MARKS-70

Q-1 Choose correct answer

[10]

1. The Op-amp is device that can be used to amplify ___ signal.
(A) D.C as well A.C (C) A.C
(B) D.C (D) None of above
2. The Resistance Measure between output terminal and ground is called ___
(A) Input voltage gain (C) CMRR
(B) Open loop voltage gain (D) none of above
3. The average of two base current entering into terminal is called ___
(A) Input offset Current (C) Input Bias Current
(B) Input offset Voltage (D) none of above
4. The differential D.C Op-Amp is mostly used to amplify output of ___
(A) High Pass filter (C) Transducer
(B) Low Pass filter (D) none of above
5. Current to Voltage Converter Op-Amp is also known as ___ op-Amp.
(A) Trans-resistive (C) Trans-inductive
(B) Trans-Capacitive (D) none of above
6. The Output voltage followed the input Voltage known as ___
(A) A.C Voltage follower (C) D.C Voltage follower
(B) Differential D.C Op-Amp (D) none of above
7. A PWM produces a train of pulse that is proportional to the ___ of modulation signal.
(A) Amplitude (C) Pulse
(B) Amplitude And Pulse (D) none of above
8. In Astable Multivibrator total Periodic time $T=T_1+T_2=$ ___
(A) $RC \log \left[\frac{(1+A)}{(1-A)} \right]$ (C) $2RC \log \left[\frac{(1+A)}{(1-A)} \right]$
(B) $2RC \log \left[\frac{(1-A)}{(1+A)} \right]$ (D) none of above
9. A ___ in general is one which Separates, unwanted quantity from the signal.
(A) filter (C) Active filter
(B) Passive filter (D) none of above
10. Bandpass filter will eliminate ___
(A) Intermediate (C) Zero
(B) Low And High (D) none of above

Q-2 Short answer type question. (any ten)

[20]

1. Briefly Explain Input Impedance And Common Mode Rejection Ratio (CMRR) of operational Amplifier.
2. Explain Ideal Op-Amp Characteristics.
3. Define Open loop frequency Response And Bandwidth.
4. Draw the Circuit Diagram of Current to Voltage Converter in Operational Amplifier.
5. Briefly explain adding Integrator with necessary figure.
6. Briefly Explain Basic Comparator in Operational Amplifier.
7. Draw Phase Detector Circuit and briefly explain it.
8. Draw Circuit of Square wave generator and briefly Explain.
9. Briefly Explain Schmitt Trigger Circuit.

10. Differentiate between Active filter Vs. Passive Filter.
11. Briefly explain Notch filter.
12. Draw the Block diagram of Op-Amp

Q.3 Draw the Circuit Diagram of Inverting Amplifier and Derive necessary expression for it with feedback. [10]

OR

Q.3(A) Describe summing op-amp with necessary diagram. [07]

Q.3(B) List the D.C and A.C Parameters of Op-Amp [03]

Q.4(A) Draw the circuit diagram and wave form of integrator using Op-Amp and explain in detail. [07]

Q.4(B) Explain D.C voltage follower Circuit. [03]

OR

Q.4 Explain in Detail Voltage to Current Converter using Op-Amp. [10]

Q.5 Describe Astable Multivibrator with Diagram and Waveform s. [10]

OR

Q.5(A) Explain Zero-Crossing Detector with necessary wave form. [07]

Q.5(B) Discuss Pulse with Modulation circuit. [03]

Q.6 Give the details about the Data Acquisition using Instrumentation Amplifier [10]

OR

Q.6 Define Instrumentation amplifier and explain it with circuit Diagram [10]

