

[52]

No. of Printed Pages: 02

**SARDAR PATEL UNIVERSITY**  
**M.Sc. (Electronics & Communication) (Semester-II) Examination**  
**Day & Date: Saturday, 25-04-2015**  
**Time: 2:30 p.m. to 5:30 p.m.**  
**Subject: Digital Electronics**  
**Paper No. PS02CELC03**

**Instructions:**

**Marks: 70**

--Figures to the right indicate marks.

**Q-1 Choose the correct answer. [8]**

1. How many binary numbers are created with 8-bits?  
a) 512                      b) 256                      c) 128                      d) 64
2. In MSI the number of gate circuit per chip is \_\_\_\_\_.  
a) <6                      b) <12                      c) <100                      d) <1000
3. An n variable K-map have \_\_\_\_\_.  
a)  $2^n$  cells                      b)  $n^2$  cells                      c)  $n^n$  cells                      d)  $n^{2n}$  cells
4. An Eight square eliminate \_\_\_\_\_ variable.  
a) 3                      b) 4                      c) 5                      d) 6
5. A \_\_\_\_\_ is a logic circuit that compares the magnitude of 2-bit binary number.  
a) 1-bit magnitude comparator                      b) 2-bit magnitude comparator  
c) 3-bit magnitude comparator                      d) 4-bit magnitude comparator
6. A Johnson counter has a initial state  $Q_1=1, Q_2=0, Q_3=0, Q_4=0$ , What will be the state of  $Q_1, Q_2, Q_3, Q_4$  output of the counter after the 7<sup>th</sup> clock pulses.  
a) 1110                      b) 1100                      c) 0000                      d) 0001
7. In RS flip-flop  $R=S=1$ , the state  $Q_{n+1}$  of the flip flop after the clock pulse will be \_\_\_\_\_.  
a) reset                      b) set                      c) indeterminate                      d) no change
8. An 8-bit synchronous counter uses flip-flop with propagation delay time of 100 ns each. The maximum possibilities time required for change of state will be \_\_\_\_\_.  
a) 100 ns                      b) 75ns                      c) 50ns                      d) 25ns

**Q-2 Answer in short. (Any SEVEN) [14]**

1. How BCD addition is performed?
2. What is meant by weighted and Non-weighted codes?
3. State De-Morgan first and second theorem.
4. What is K-map? What are the advantages and disadvantages of it's?
5. Which gates are called universal building blocks? Why?
6. Explain 1-bit magnitude comparator.
7. Explain RS flip-flop.
8. What is shift register? What is the basic difference between shift register and counter?
9. Give the difference between Serial and Parallel counter.

(P.T.O)

- Q-3 (a) Perform the following. (6)
- (I) Convert  $(105.15)_{10}$  to binary.
  - (II) Convert  $(4057.06)_8$  to decimal.
  - (III) Convert  $(110101.101010)_2$  to octal.

(b) With necessary circuit diagram explain Johnson counter. (6)

OR

(b) With necessary circuit diagram, truth table and waveforms explain MOD-8 synchronous counter. (6)

Q-4 (a) Reduce the expression  $F = \sum M(0, 2, 3, 4, 5, 6)$  by SOP and implement in to NAND logic. (6)

(b) Perform the following. (6)

(I) Subtract 14 from 46 using 8-bit 2's complement method.

(II) Perform the XS-3 addition of 37 and 28.

(III) Find the 10's Complement of the 4069.

OR

(b) Reduce the expression  $F = \sum m(0, 1, 2, 5, 8, 9, 10)$  by SOP. Also count how many inputs required by the converting in to simple logic circuit. (6)

Q-5 (a) Reduce the following Boolean expression:  $\overline{\overline{AB} + ABC + A(B + \overline{AB})}$  (6)

(b) Perform the following. (6)

(I) Subtract 15 from 38 using BCD subtraction method.

(II) Subtract 27 from 57 using XS-3 code.

(III) Convert gray 111001 to binary.

OR

(b) Explain 2-bit magnitude comparator in detail with necessary diagram. (6)

Q-6 (a) Explain edge triggered D flip-flop in detail. (6)

(b) What is PLA? Show how PLA circuit can be programmed to implement the 3-bit binary to Gray converter. (6)

OR

(b) Give detail account of Master slave JK flip-flop. (6)

—X—