

(7)

Sc

SARDAR PATEL UNIVERSITY

M. Sc. IT (Integrated) SEM - II Examination

Subject: - Digital Electronics

Course: PS02EIIIT01

Max. Marks : 70

Date: 2/05/2015

Time: 2:30 pm to 4:30 pm

Q.1 Select best option from the following multiple choice questions. [10]

1. A combinational circuit that performs the arithmetic addition of two bits is called _____.
(a) Half Adder (b) Full Adder
(c) Binary Adder (d) Decoder
2. Half adder consists of _____ and _____ Gates.
(a) XNOR, AND (b) XNOR, OR
(c) XOR, AND (d) XOR, OR
3. A _____ is a combinational circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.
(a) Half Adder (b) Encoder
(c) Decoder (d) Comparator
4. A 8 - to - 1 line multiplexer requires _____ data select line.
(a) 1 (b) 2
(c) 3 (d) 4
5. Which of the following device has many input and one output?
(a) Flip-flop (b) Multiplexer
(c) De-multiplexer (d) Counter
6. A Comparator compares how many words?
(a) 1 (b) 2
(c) 3 (d) 4
7. In K-Map, Quad eliminates _____ variable.
(a) 2 (b) 4
(c) 8 (d) 16
8. Don't care conditions are marked as _____ in the output column of the function table.
(a) 0 (b) 1
(c) X (d) None of these
9. The basic storage element in a digital system is _____.
(a) Flip-flop (b) Multiplexer
(c) Encoder (d) Counter
10. Which of the following is Universal Flip-flop?
(a) J-K Flip-flop (b) R-S Flip-flop
(c) D Flip-flop (d) Master-Slave Flip-flop

- Q. 2 Write Short Answer Questions: Attempt any Ten [20]
1. Explain De-Morgan First Theorem.
 2. Explain Binary Adder.
 3. Explain Binary Subtractor.
 4. Draw the circuit diagram of Nibble Multiplexer.
 5. Draw the circuit diagram of 1 X 4 Line De-Multiplexer.
 6. Draw the circuit diagram of Comparator.
 7. What is K-Map?
 8. Explain Sum of Product (SOP).
 9. Explain Pair with example.
 10. Explain Shift Left with example.
 11. Explain Shift Right with example.
 12. Draw the circuit of D Flip Flop.
- Q.3 A. Explain Half Adder in detail. [5]
 B. Explain 3 X 8 Line Decoder in detail. [5]
- OR**
- Q.3 A. Explain Full Adder in detail. [5]
 B. Explain 8 X 3 Line Encoder in detail. [5]
- Q.4 What is Decoder? Explain Seven Segment Decoder in detail. [10]
- OR**
- Q.4 What is Multiplexer? Explain 8 X 1 Line Multiplexer in detail. [10]
- Q.5 A Explain Quad and Octet in K-Map with example. [4]
 B. Simplify the following Boolean Function using K-Map.

$$F (A, B, C, D) = \sum (1, 2, 5, 6, 8, 12, 14)$$
 [6]
- OR**
- Q.5 A. Explain Don't Care Condition in detail. [4]
 B. Simplify the following Boolean Function using K-Map.

$$F (A, B, C, D) = \sum (1, 3, 5, 6, 8, 11, 15)$$
 [6]
- Q.6 A. Explain RS Flip Flop in detail. [5]
 B. Explain Ring Counter in detail. [5]
- OR**
- Q.6 A. Explain JK Flip Flop in detail. [5]
 B. Explain Control Buffer Register in detail. [5]

-x-