

[56]

No. of Printed Pages:2

**SARDAR PATEL UNIVERSITY**  
**M.Sc. (PHYSICS) (II Semester) Examination**  
**Tuesday, 12<sup>th</sup> April, 2016 10:30 am to 1:30 pm**  
**Course No.: PS02EPHY01**  
**ANALOG AND DIGITAL ELECTRONICS**

**Total Marks:70**

- Q.1** Eight multiple choice questions (MCQ) carrying one mark each. Show (8) your choice of answer against the question Number.
- (i) Which resistance in UJT is static resistance?  
(a) Emitter – Base:1      (b) Emitter – Base:2  
(c) Base:1 – Base:2      (d) None
  - (ii) In a transistor when emitter junction and collector junction are both forward biased than region of operation is  
(a) Saturation      (b) Active  
(c) cut-off      (d) Inverted
  - (iii) When a diode operates in I<sup>st</sup> and III<sup>rd</sup> quadrant of its I-V characteristics, then \_\_\_\_\_  
(a)Energy is absorbed by the diode,      (b)Energy is given by the diode  
(c)No energy transfer is taking place,      (d)None of them
  - (iv) Which device consists of four consecutive alternative semiconductor layers?  
(a) Photodiode      (b) Phototransistor  
(c) Solar cell      (d) Silicon Control Rectifier
  - (v) Data is said to be in parallel form if the bits are available  
(a) Simultaneously      (b) Sequentially  
(c) Both a and b      (d) None
  - (vi) A counter circuit in which all Flip-Flops change the states simultaneously is known as  
(a) Up-Counter      (b) Down Counter  
(c) Synchronous Counter      (d) Asynchronous Counter
  - (vii) Which of the following circuits is a device whose inputs are decimal digits and/or alphanumeric characters and outputs are the coded representation of those inputs?  
(a) Multiplexer      (b) Adder      (c) Encoder,      (d) De-multiplexer
  - (viii) Which of the following logic circuits is used for data selection and parallel-to-serial conversion  
(a) Multiplexer,      (b) Decoder,      (c) Encoder,      (d) De-multiplexer
- Q.2** Short answer questions carrying two marks each (14)  
(attempt any seven out of nine).
- (i) What do you understand by dead zone in a series noise clipper?      PTO
  - (ii) Why direct bandgap materials are used for the fabrication of light emitting diode (LED)?

- (iii) How a diode is used as switch?
- (iv) Draw a Karnaugh map for the expression  $\sum_m (0,2,4,6,7,8,10)$  and solve it.
- (v) Distinguish between Asynchronous and Synchronous counters.
- (vi) Explain the use of Enable input/s of a counter.
- (vii) Define Resolution and Accuracy of DAC.
- (viii) Why does the conversion time increase with the value of the analog input voltage in a counter type ADC?
- (ix) How are ROMs and RAMs classified?

- Q.3(a) Explain in detail the construction and working of astable multivibrator using IC-555. (6)
- (b) Write a short note on BCD code. (6)

OR

- (b) With suitable schematic diagram, describe in details the internal circuit diagram and working of IC-555 timer. (6)

- Q.4(a) With necessary circuit diagram explain the working of negative and positive clamping circuit. (6)

- (b) Draw the block diagram, equivalent circuit diagram and static emitter characteristic curve of UJT and explain its working. (6)

OR

- (b) Write a short note on solar cell. (6)

- Q.5(a) Write a short note on semiconductor memory. (6)

- (b) What are encoder and decoder circuits? Explain any one of them in detail and write its applications. (6)

OR

- (b) With the help of logic and timing diagram explain the operation of an asynchronous type 2-bit ripple Up-counter using positive edge triggered Flip-Flops. (6)

- Q.6(a) Sketch an architectural block-diagram of 8085 microprocessor and explain the role of its each block in brief. (6)

- (b) Explain in detail how Digital to Analog conversion takes place using R-2R ladder network type DAC circuit. (6)

OR

- (b) With the help of neat diagram explain the ADC by the counter type A/D converter. State its advantages and limitations. (6)

XXXXXXXXXX